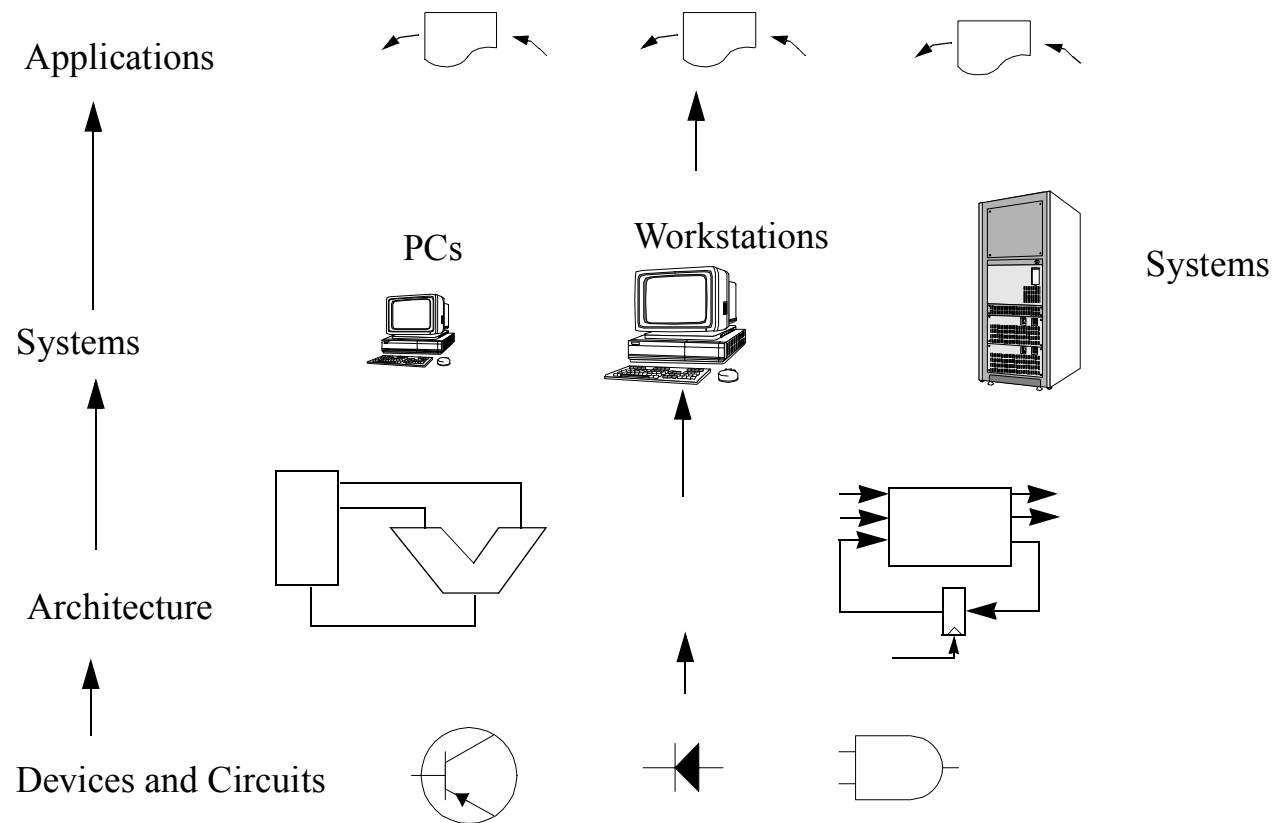


COMP3222/9222 Digital Circuits & Systems


8. VHDL for Simulation

Describing Digital Systems



- Systems are described at multiple levels of abstraction

Hardware Description Languages

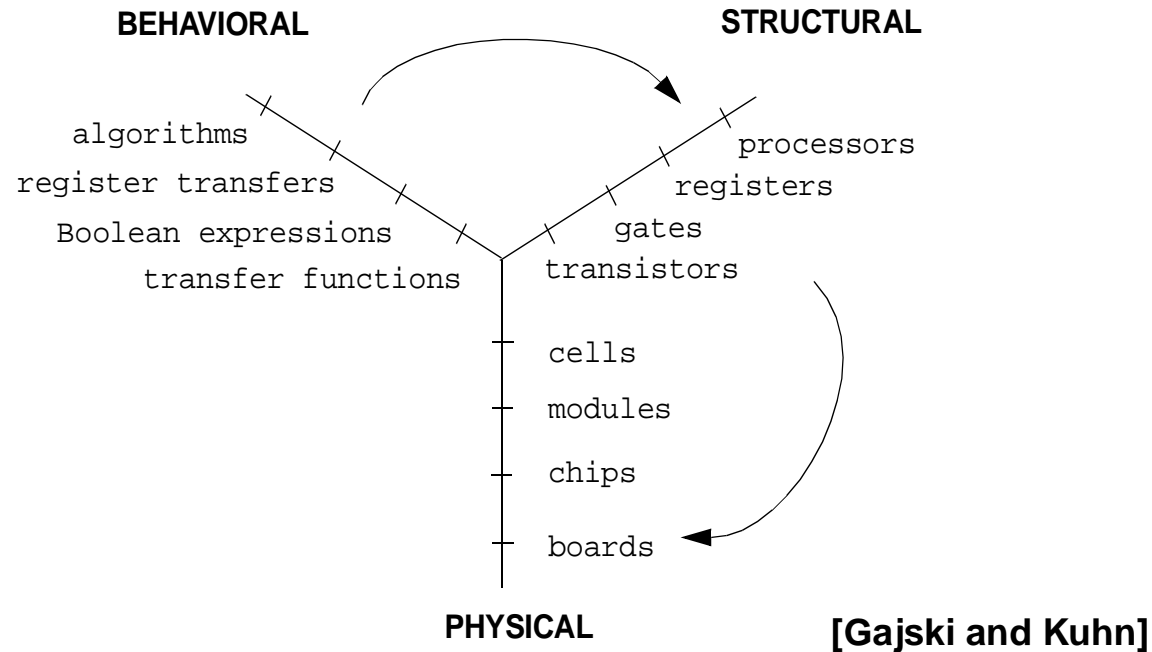


- And design is structured around a hierarchy of representations
- HDLs can describe distinct aspects of a design at multiple levels of abstraction


Design description has multiple purposes

- Design Specification
 - unambiguous definition of components and interfaces in a large design
- Design Simulation
 - verify system/subsystem/chip performance prior to design implementation
- Design Synthesis
 - automated generation of hardware

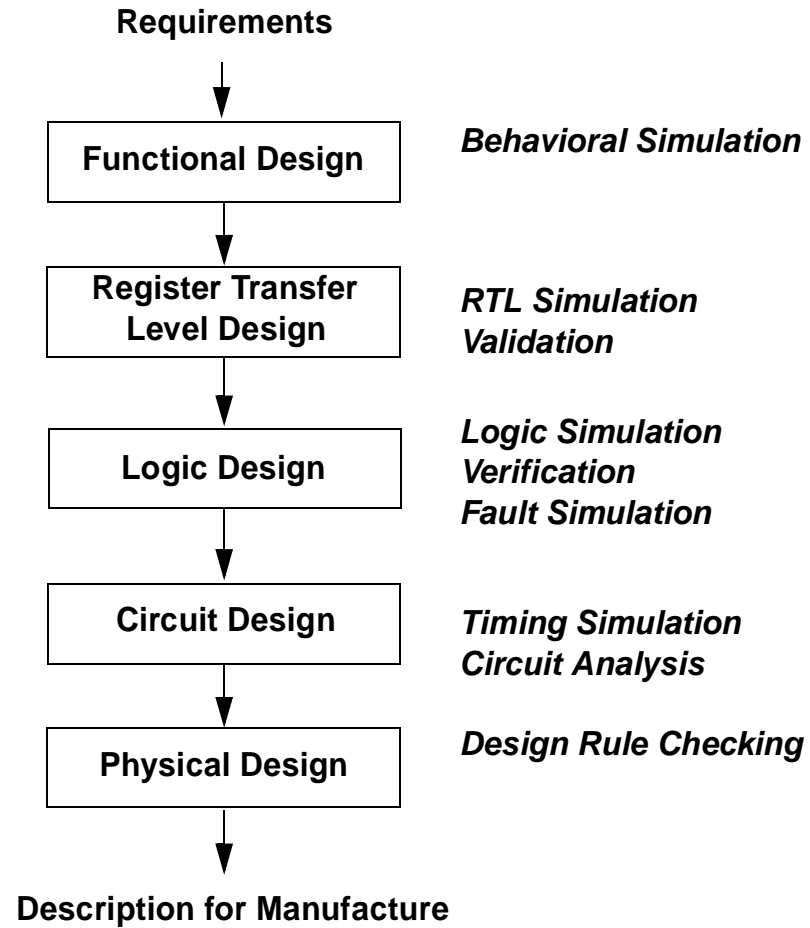Simulation in the digital system design process




Role of VHDL

 


- System description and documentation
- System simulation <= focus of this lecture
- System synthesis <= overall concern of this course!

Behavioral Attributes of Digital Systems

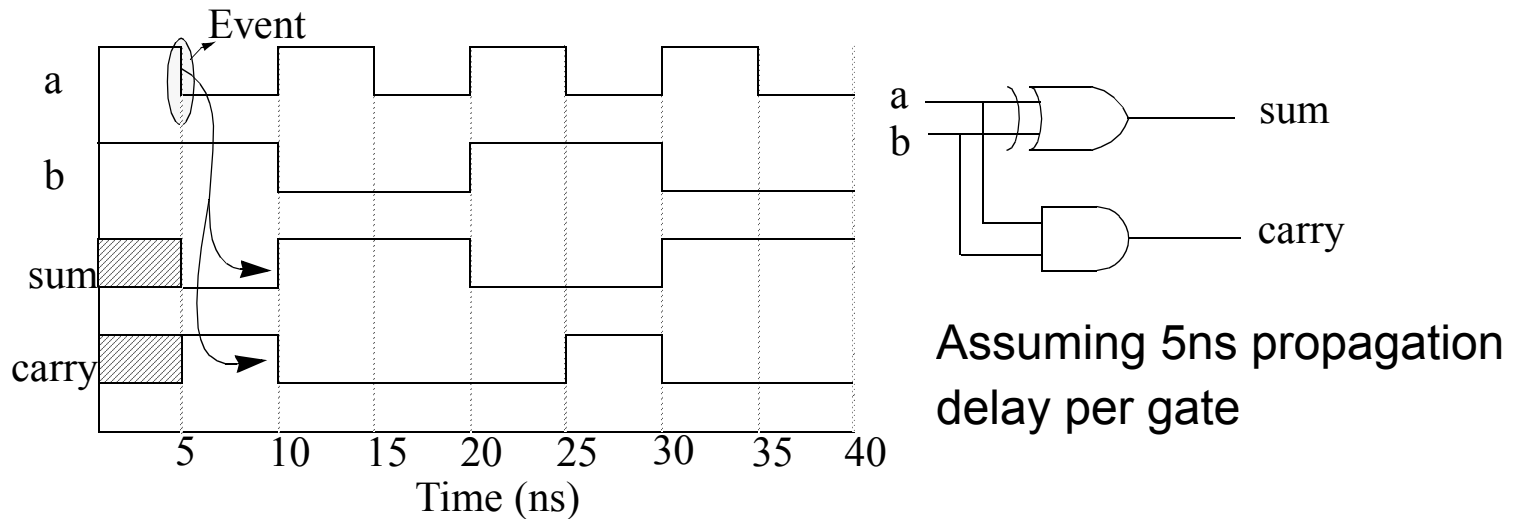


- Digital systems are concerned with *signals* and their *values*
- *Events, propagation delays, concurrency*
- The time-ordered sequence of events produces a *waveform*

Simulation Modeling

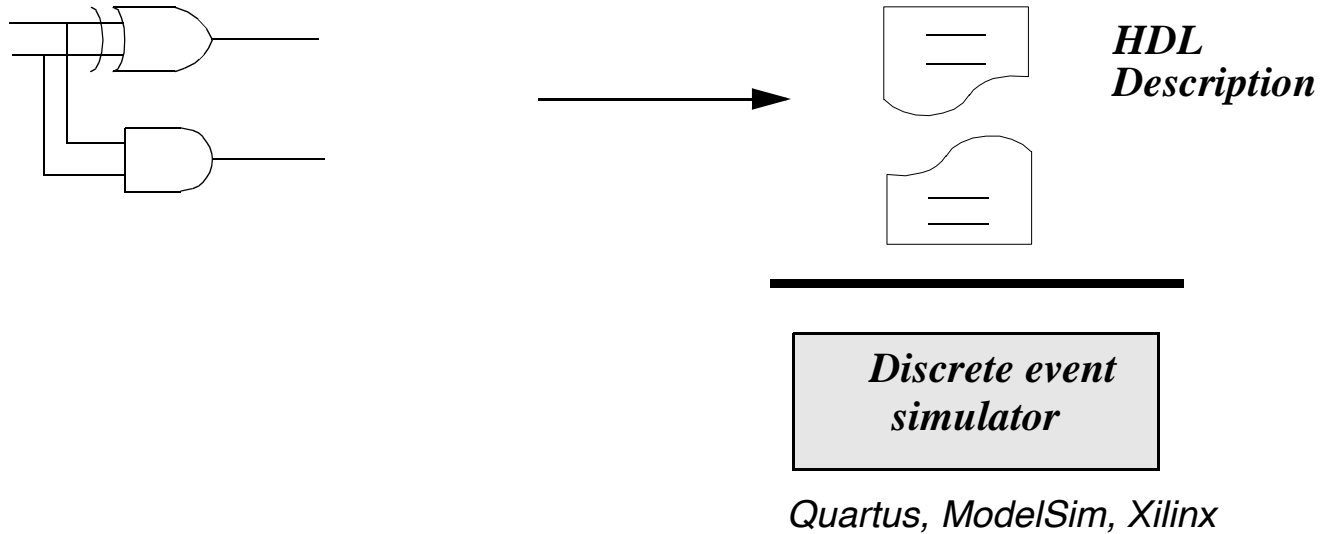


- VHDL designs describe the generation of events in digital systems
- A discrete event simulator manages event ordering and the progression of time

Simulation of Digital Systems

 

- Digital systems propagate events
- Discrete event simulations manage the generation and recording of events

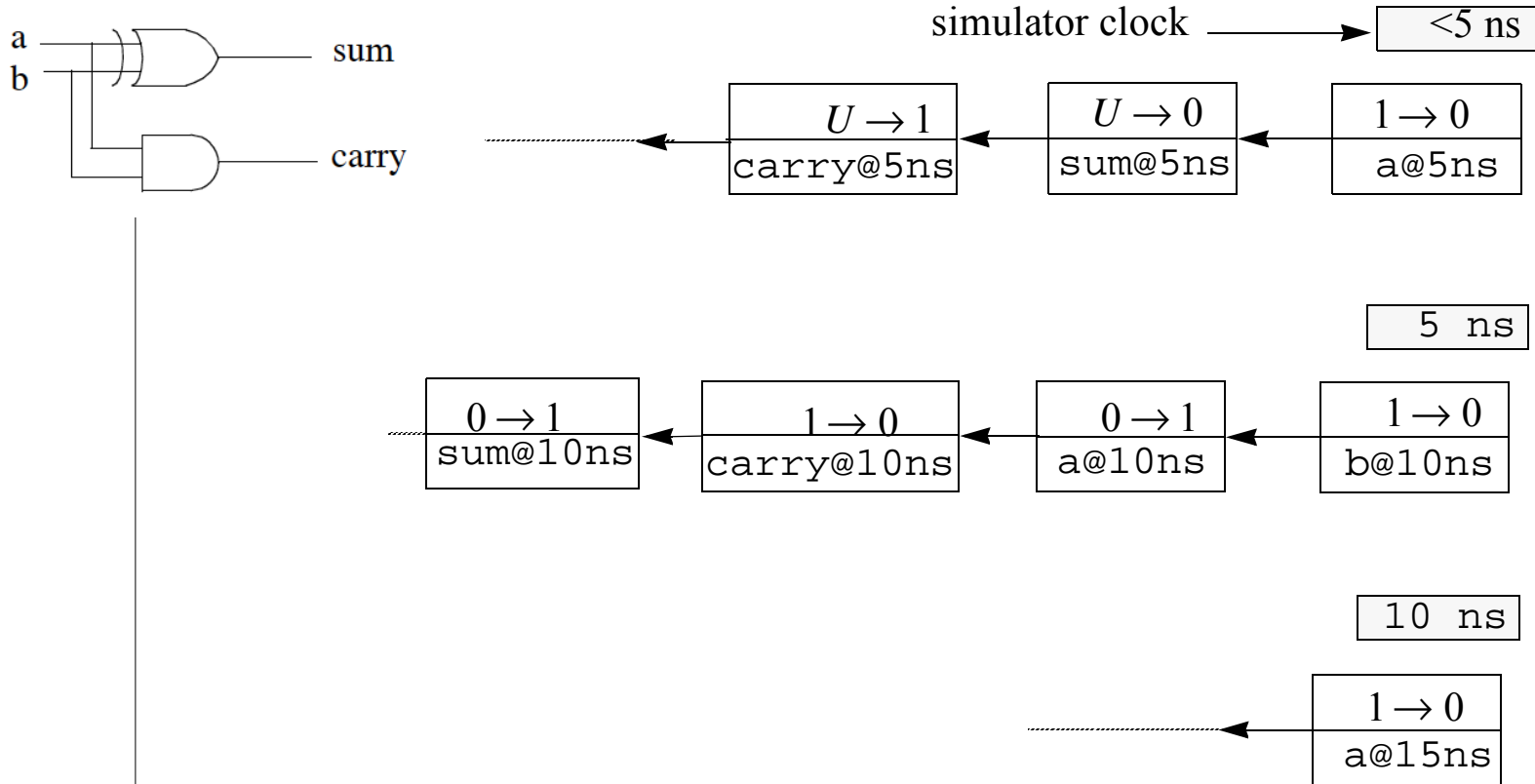Discrete Event Simulation: Half Adder Model




- Assume *a* & *b* are set to 1 initially and the gates have 5ns propagation delay
- Management of simulation time and ordering of events
- Two step model of the progression of time

Modeling Digital Systems

- VHDL programs describe behavioral attributes of digital systems
 - events, propagation delays, concurrency
 - waveforms and timing
 - signal values
- Discrete event simulators mimic the operation of the system being described using a two step model of time
 - 1. assign values scheduled for signals at the current time
 - 2. process affected components and schedule future signal values
- This ensure events are generated and processed in the correct order
- And that *only and all* those events that would have been generated in the physical system are generated

Understanding delays

 

- Inertial delay model
- Transport delay model
- Delta delay model

Understanding Delays

- Inertial delay
 - default delay model
 - suitable for modeling delays through devices such as gates
 - only propagates input pulses longer than the inertial delay
- Transport Delay
 - models delays through devices with very small inertia, e.g, wires
 - all input events are propagated to output signals
- Delta delay
 - used when propagation delays are not specified
 - infinitesimally small delays are automatically inserted by the simulator to preserve the correct ordering of events

Inertial & Transport Delays: Example

architecture transport_delay of

half_adder is

signal s1, s2: std_logic := '0';

begin



s1 <= (a xor b) **after 2 ns; -- inertial delay**

s2 <= (a and b) **after 2 ns;**

sum <= **transport s1 after 4 ns;**

carry <= **transport s2 after 4 ns; -- transport delay**


end transport_delay;

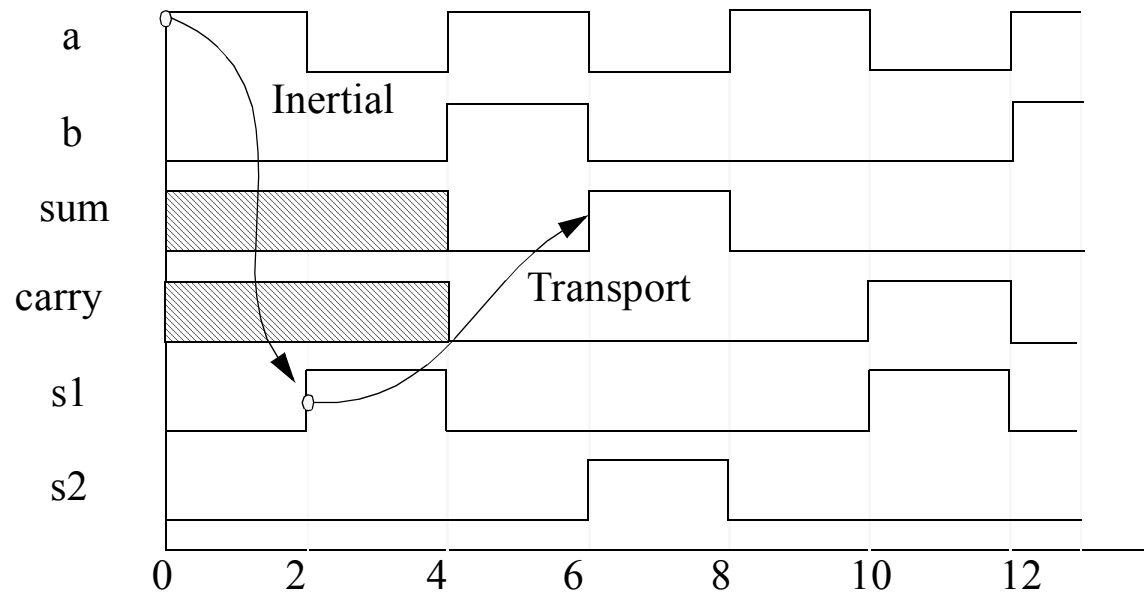 



Delta Delays: Example

```
library IEEE;  
use IEEE.std_logic_1164.all;  
entity combinational is  
  port (In1, In2: in std_logic;  
        z : out std_logic);  
end combinational;
```

 
```
architecture behavior of  
combinational is  
  signal s1, s2, s3, s4: std_logic:= '0';  
begin  
  s1 <= not In1;  
  s2 <= not In2;  
  s3 <= not (s1 and In2);  
  s4 <= not (s2 and In1);  
  z <= not (s3 and s4);  
end behavior;
```



Delta Delays: Example

  


Simulating a 4-to-1 multiplexer

 

(a) Graphic symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table

 

(c) Circuit

Q1: Assuming $s_1 = s_0 = 0$; $w_0 = w_2 = 0$; and $w_1 = w_3 = 1$, sketch the delta transitions of all affected signals if s_0 transitions from $0 \rightarrow 1$ @ 10ns; depict the state of the event queue prior to each transition.

Q2: Repeat Q1 assuming gates have a 2ns inertial delay and wires have a 1ns transport delay