

COMP3222/9222 Digital Circuits & Systems


5. Flip-flops, Registers, Counters

Objectives

- Learn about logic circuits that store information
 - Flip-flops that store a single bit
 - Registers that store multiple bits
 - Shift registers that shift the contents of the register
 - Counters of various types
- VHDL constructs used to implement storage elements

Why we need circuits with memory

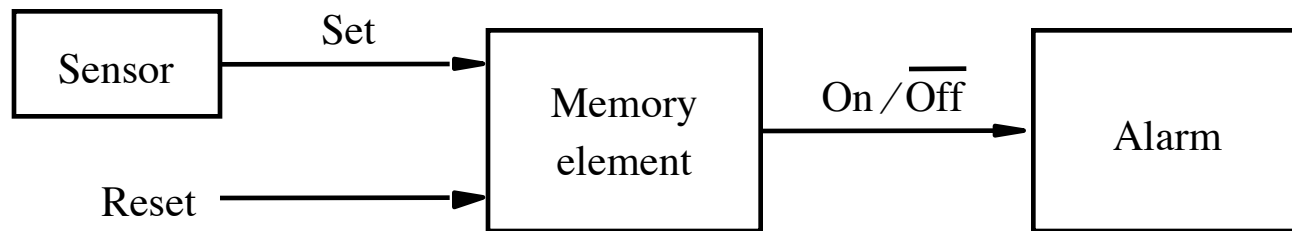
- Consider an alarm system that is required to remain activated when triggered, even when the cause for triggering has ceased



- Here, the *Reset* signal is intended to provide a means of switching off the alarm

How do we create a memory element?


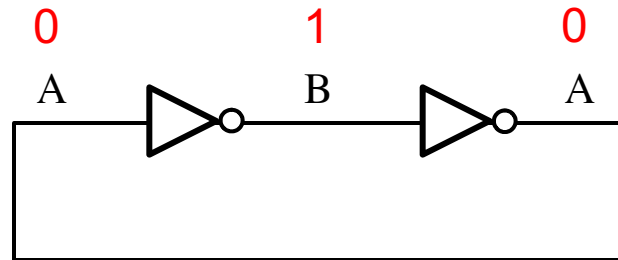
- Use feedback to “trap” a value
- Consider a simple cyclic circuit comprising two inverters




- The circuit has two stable states
- But there is no way of changing from one state to the other

A controlled memory element

0 = preserve current state

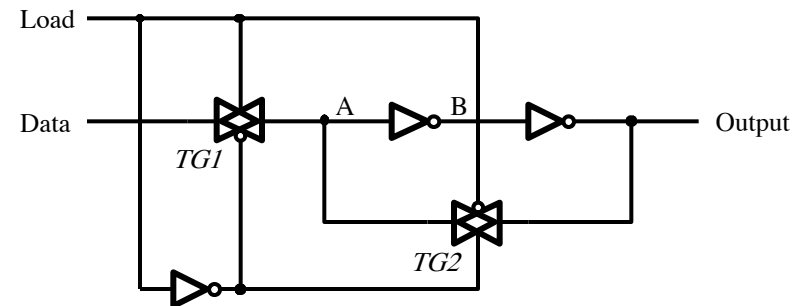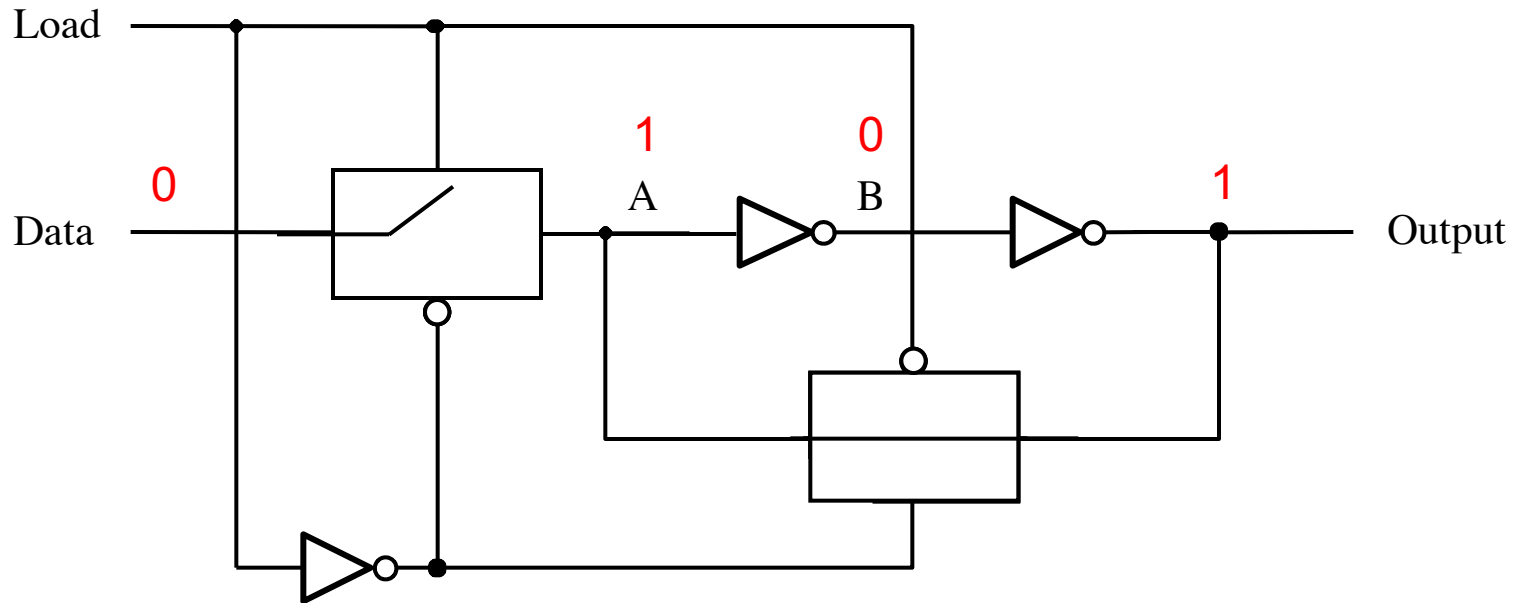



A memory element with NOR gates

 

A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

- When both *Set* and *Reset* are 0, the state, *Q*, is preserved
- $Set = 1, Reset = 0 \Rightarrow Q = 1$
- $Set = 0, Reset = 1 \Rightarrow Q = 0$
- Known as a *latch*

 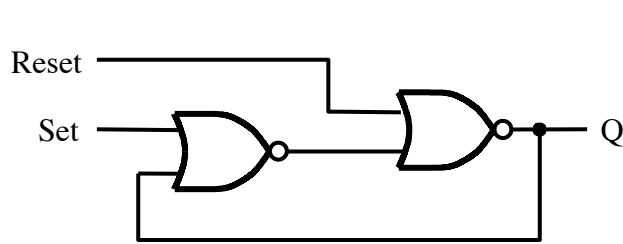
Basic latch using cross-coupled NOR gates



S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(a) Conventional circuit diagram


(b) Characteristic table

 

Oscillatory behaviour which settles to a final state that depends upon the relative speed of gates and wires

Gated SR latch

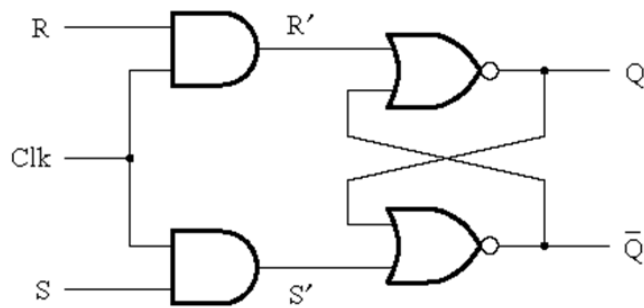- A control input (Clk) acts to enable state changes




(a) Circuit


Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

 (b) Characteristic table

Illegal input condition as outputs are supposed to be complements of each other




(c) Timing diagram

 

 (d) Graphical symbol

Gated SR latch with NAND gates

- More usual configuration as it uses less transistors
 - Has exactly the same characteristic table
 - Note that S & R inputs are flipped about wrt the outputs




Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

(b) Characteristic table

A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0

Gated D latch

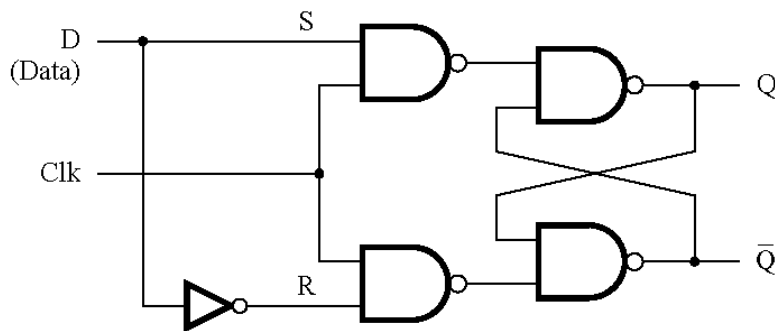
- Eliminates the illegal input combination $S = R = 1$
- Useful for storing a data bit




(a) Circuit

Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

(b) Characteristic table

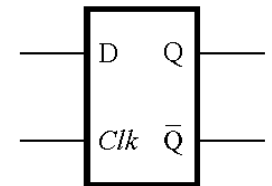

(c) Graphical symbol

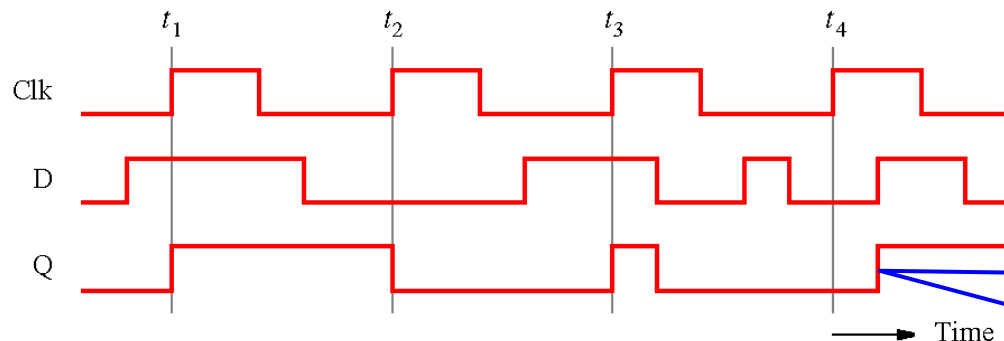


(d) Timing diagram

latches are said to be "transparent" to changes in the data input while the *Clk* input is high


Negative edge-triggered (Master-slave) D flip-flop

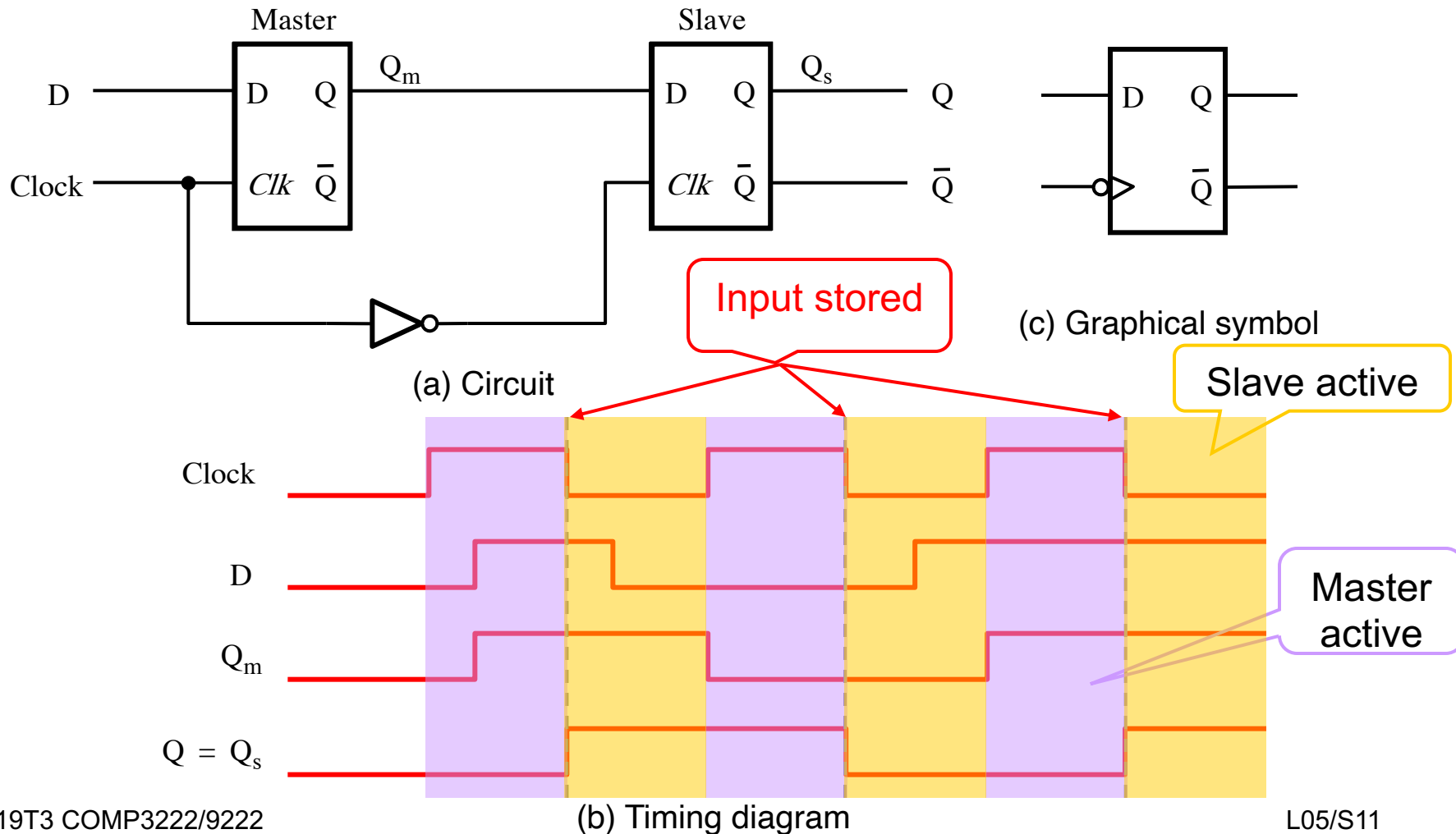- Latches are triggered by the level of the control signal, flip-flops are triggered on control signal transitions



A positive-edge-triggered D flip-flop

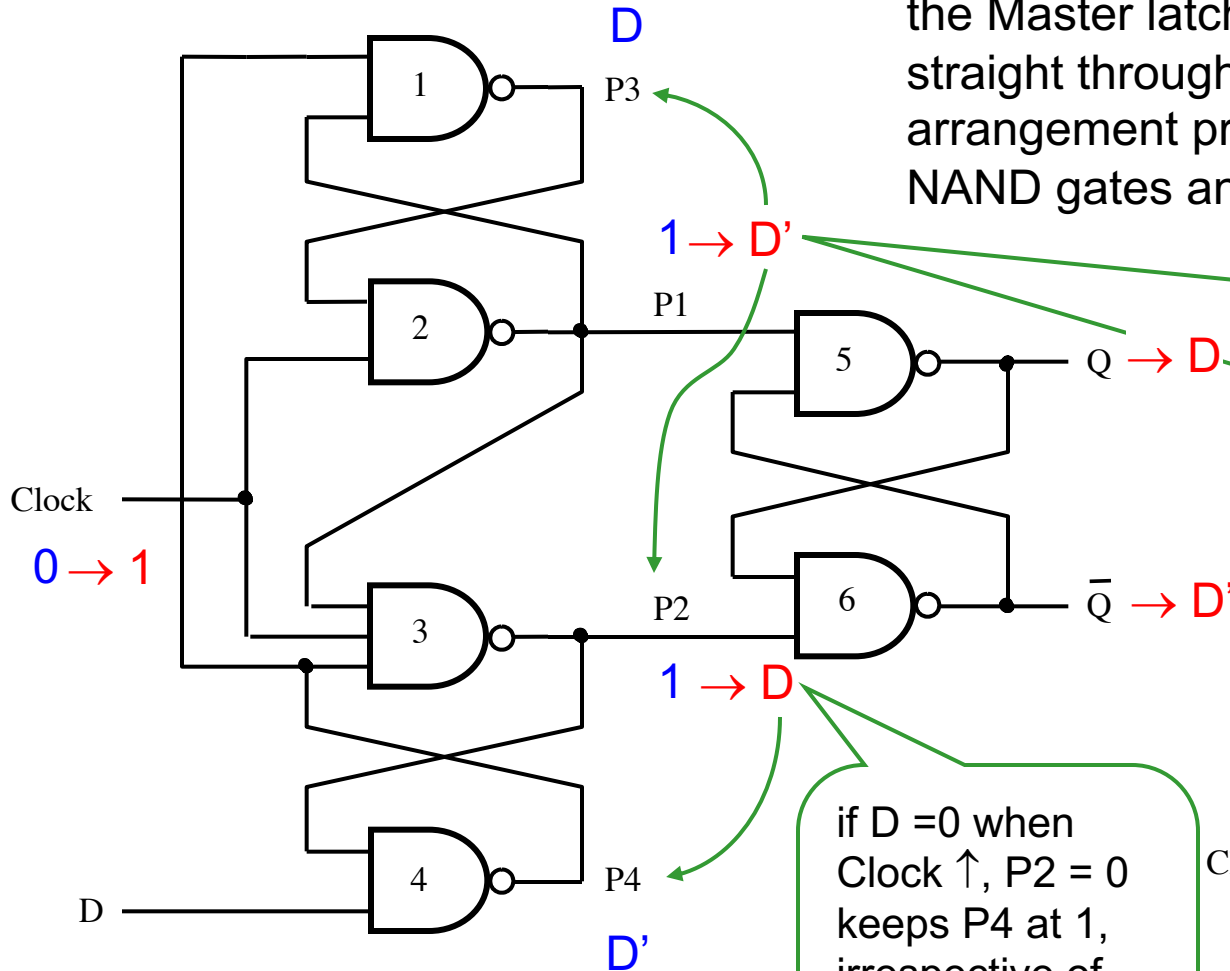
We could just invert the *Clk* input to the Master latch and feed the *Clk* signal straight through to the Slave, but the arrangement presented here saves two NAND gates and two inverters



 (a) Circuit


if $D = 1$ when $\text{Clock} \uparrow$, $P1 = 0$ keeps $P2$ & $P3$ at 1, irrespective of subsequent changes to D while Clock high

if $D = 0$ when $\text{Clock} \uparrow$, $P2 = 0$ keeps $P4$ at 1, irrespective of subsequent changes to D while Clock high




 (b) Graphical symbol

Comparison of level-sensitive and edge-triggered D-type storage elements



(a) Circuit

 

(b) Timing diagram

Recall the specification of implied memory



```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY implied IS  
    PORT ( A, B      : IN    STD_LOGIC ;  
          AeqB      : OUT  STD_LOGIC ) ;  
END implied ;
```

```
ARCHITECTURE Behavior OF implied IS  
BEGIN
```

```
    PROCESS ( A, B )  
    BEGIN  
        IF A = B THEN  
            AeqB <= '1' ;  
        END IF ;  
    END PROCESS ;
```

```
END Behavior ;
```

  

Resulting circuit has to remember the value of AeqB when $A \neq B$


Code for a gated D latch

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY latch IS
    PORT ( D, CLK : IN      STD_LOGIC ;
          Q       : OUT  STD_LOGIC);
END latch ;

ARCHITECTURE Behavior OF latch IS
BEGIN
    PROCESS ( D, CLK )
    BEGIN
        IF CLK = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

 *Note: the PROCESS describing a latch, while exploiting *implicit memory*, complies with the *COMBINATIONAL* design rule that all signals that can affect the output are listed in the sensitivity list; otherwise (if you only list the CLK signal) the compiler will think you are specifying a weird kind of flip-flop!*



Code for a positive edge-triggered D flip-flop


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, CLK : IN    STD_LOGIC ;
          Q       : OUT STD_LOGIC ) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( CLK )
    BEGIN
        IF CLK'event AND CLK = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

The boolean signal attribute
'event' is true when the signal
transitions from 0→1 or 1→0

 Notes: (i) *SYNCHRONOUS PROCESSES* only list the CLK signal in the sensitivity list;
(ii) All assignment statements within a synchronous process should be guarded by an IF CLK'event AND CLK='1'... condition;
(iii) Each signal on the LHS of an assignment statement guarded by an IF CLK'event AND CLK='1'... condition is the output of a flip-flop



Equivalent code using a WAIT UNTIL statement

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```


```
ENTITY flipflop IS  
    PORT ( D, Clock      : IN STD_LOGIC ;  
          Q              : OUT  STD_LOGIC );  
END flipflop ;
```

```
ARCHITECTURE Behavior OF flipflop IS  
BEGIN  
    PROCESS  
    BEGIN  
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;  
        Q <= D ;  
    END PROCESS ;  
END Behavior ;
```


When used for synthesis,
the WAIT UNTIL
statement must be the
first in a PROCESS block;
all assignment statements
that follow infer a flip-flop

Master-slave D flip-flop with *Clear* and *Preset*

 - A design may call for a preset value on a FF
- Active low *Preset'* and *Clear'* inputs allow the flip-flop to be set to a given value asynchronously (independently of the *Clock*) – only one of them should be pulled low at a time




(a) Circuit

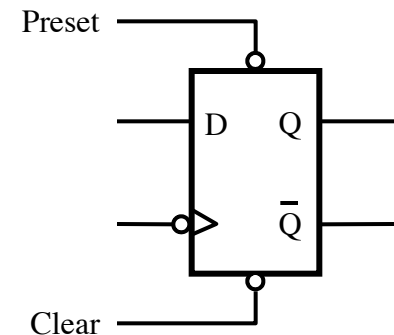

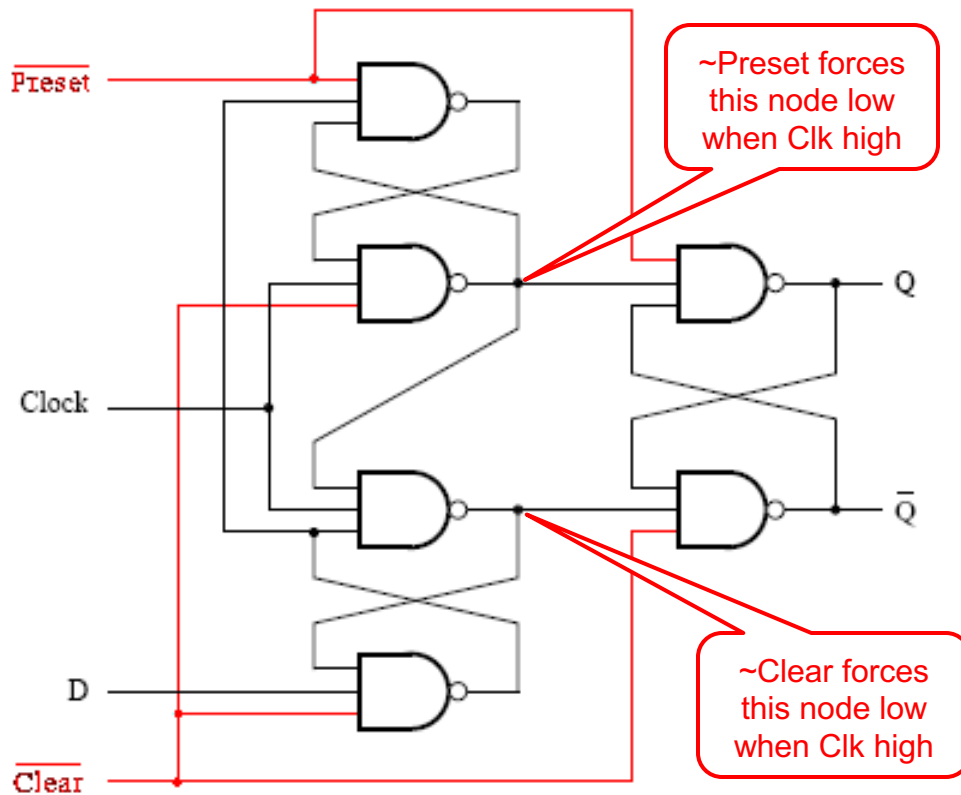
(b) Graphical symbol

- How long does the FF stay in the Clear or Preset state?

Positive-edge-triggered D flip-flop with *Clear* and *Preset*




(a) Circuit

 

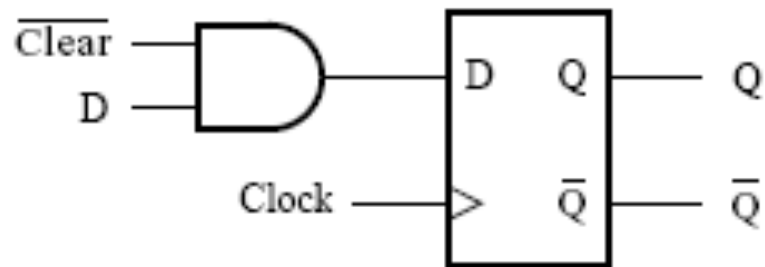(b) Graphical symbol

Positive-edge-triggered D flip-flop with synchronous *Clear* and *Preset*

- Synchronous clear and preset is best done by gating the *D* input



D flip-flop with asynchronous reset

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY flipflop IS  
    PORT ( D, Resetn, CLK : IN      STD_LOGIC ;  
          Q               : OUT    STD_LOGIC) ;  
END flipflop ;
```

```
ARCHITECTURE Behavior OF flipflop IS  
BEGIN
```

```
    PROCESS ( Resetn, CLK )  
    BEGIN  
        IF Resetn = '0' THEN  
            Q <= '0' ;  
        ELSIF CLK'EVENT AND CLK = '1' THEN  
            Q <= D ;  
        END IF ;  
    END PROCESS ;
```

```
END Behavior ;
```

Notes: (i) For a synchronous process with an asynchronous reset/set, both the CLK and the reset/set signal must be in the sensitivity list.

(ii) Only assign a '0'/'1' to the FF output within the reset/set condition.

D flip-flop with synchronous reset

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY flipflop IS  
    PORT ( D, Resetn, Clock : IN      STD_LOGIC ;  
          Q                  : OUT    STD_LOGIC) ;  
END flipflop ;
```

```
ARCHITECTURE Behavior OF flipflop IS  
BEGIN
```

```
    PROCESS  
    BEGIN
```

```
        WAIT UNTIL Clock'EVENT AND Clock = '1';
```

```
        IF Resetn = '0' THEN
```

```
            Q <= '0' ;
```

```
        ELSE
```

```
            Q <= D ;
```

```
        END IF ;
```

```
    END PROCESS ;
```

```
END Behavior ;
```

Question: Which other way could you specify this behaviour?

Code for an **eight-bit register** with asynchronous reset

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY reg8 IS
    PORT ( D           : IN      STD_LOGIC_VECTOR(7 DOWNTO 0) ;
          Resetn, Clock : IN      STD_LOGIC ;
          Q             : OUT     STD_LOGIC_VECTOR(7 DOWNTO 0) ) ;
END reg8;

ARCHITECTURE Behavior OF reg8 IS
BEGIN
    PROCESS (Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= "00000000" ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Code for an *n*-bit register with asynchronous clear

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

Parameterized component
with default value of 16 for
the data width parameter N

```
ENTITY regn IS  
    GENERIC ( N : INTEGER := 16 );  
    PORT ( D          : IN      STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;  
          Resetn, Clock : IN      STD_LOGIC ;  
          Q           : OUT     STD_LOGIC_VECTOR(N-1 DOWNTO 0) ) ;  
END regn;
```

```
ARCHITECTURE Behavior OF regn IS  
BEGIN
```

Idiom for setting all
bits of a signal to 0s

```
    PROCESS (Resetn, Clock )  
    BEGIN  
        IF Resetn = '0' THEN  
            Q <= (OTHERS => '0') ;  
        ELSIF Clock'EVENT AND Clock = '1' THEN  
            Q <= D ;  
        END IF ;  
    END PROCESS ;  
END Behavior ;
```


8-bit register based on *regn* component

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;


ENTITY reg8 IS
    PORT ( D          : IN      STD_LOGIC_VECTOR(7 DOWNTO 0) ;
          Resetn, Clk : IN      STD_LOGIC ;
          Q           : OUT     STD_LOGIC_VECTOR(7 DOWNTO 0) ) ;
END reg8 ;
```

```
ARCHITECTURE Structure OF reg8 IS
BEGIN
    reg8: regn
        GENERIC MAP ( N => 8 )
            PORT MAP ( D, Resetn, Clk, Q);
END Structure ;
```

Assumes *regn* component
declared in the working
directory


GENERIC MAP used to
overwrite default parameter
value

A simple shift register

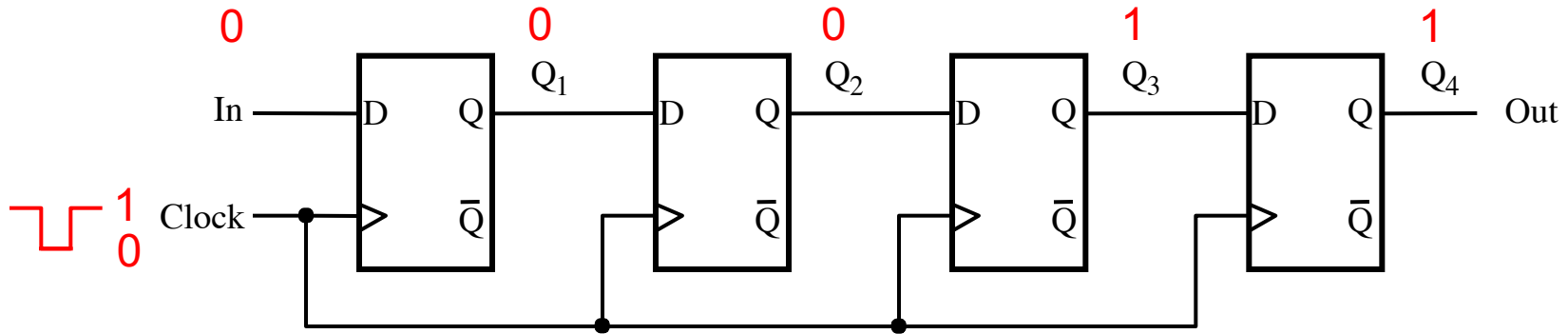

	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1

Parallel-access shift register

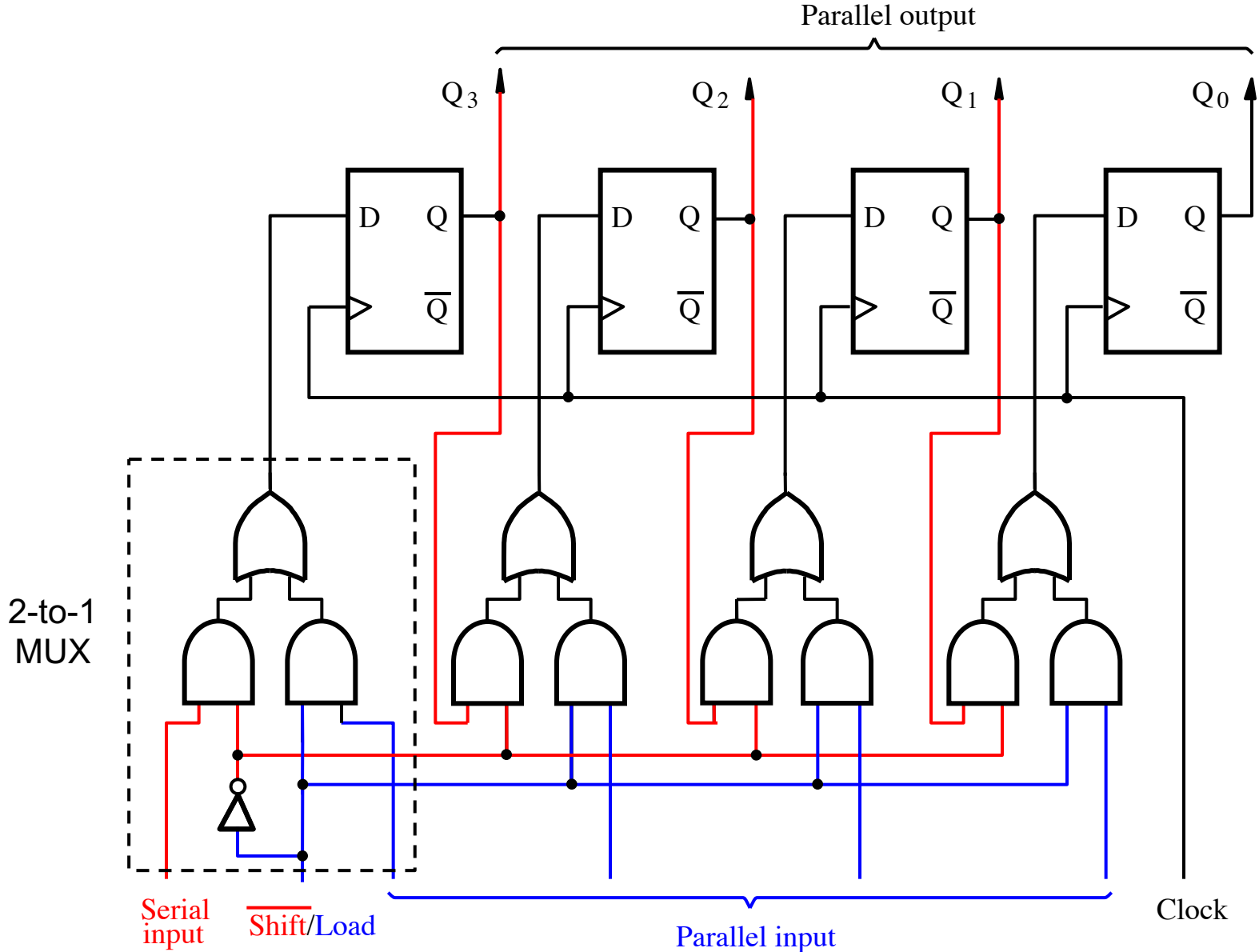

Behavioural code for a D flip-flop with a 2-to-1 multiplexer on the *D* input

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY muxdff IS
    PORT ( D0, D1, Sel, Clock : IN    STD_LOGIC ;
           Q                   : OUT  STD_LOGIC) ;
END muxdff;
```

```
ARCHITECTURE Behavior OF muxdff IS
BEGIN
```

```
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1';
        IF Sel = '0' THEN
            Q <= D0 ;
        ELSE
            Q <= D1 ;
        END IF ;
    END PROCESS ;
```

```
END Behavior ;
```

-- or:

```
-- PROCESS (Clock)
-- BEGIN
--     IF Clock' ... THEN
--         IF Sel ...
--             etc.
--     END IF;
-- END IF;
```

Hierarchical code for a four-bit shift register

- Design hierarchies are recursive *structures* comprised of components, or sub-circuits, whose architectures, at the leaf level, are expressed in terms of their behaviours


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY shift4 IS
    PORT ( R      : IN      STD_LOGIC_VECTOR( 3 DOWNT0 0) ;
          L, w, Clock : IN      STD_LOGIC ;
          Q      : BUFFER   STD_LOGIC_VECTOR( 3 DOWNT0 0) ) ;
END shift4;
```

BUFFER mode allows Q to be used in both IN and OUT modes

```
ARCHITECTURE Structure OF shift4 IS
    COMPONENT muxdff
        PORT ( D0, D1, Sel, Clock : IN  STD_LOGIC ;
              Q                  : OUT STD_LOGIC ) ;
    END COMPONENT;
BEGIN
    Stage3: muxdff PORT MAP ( w, R(3), L, Clock, Q(3) );
    Stage2: muxdff PORT MAP ( Q(3), R(2), L, Clock, Q(2) );
    Stage1: muxdff PORT MAP ( Q(2), R(1), L, Clock, Q(1) );
    Stage0: muxdff PORT MAP ( Q(1), R(0), L, Clock, Q(0) );
END Structure ;
```

Flip-flops

 

Alternative (behavioural) code for a shift register

```
1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;

3  ENTITY shift4 IS
4      PORT ( R          : IN          STD_LOGIC_VECTOR( 3 DOWNT0 0) ;
5              L, w, Clock : IN          STD_LOGIC ;
6              Q          : BUFFER     STD_LOGIC_VECTOR( 3 DOWNT0 0) ) ;
7  END shift4;

8  ARCHITECTURE Behavior OF shift4 IS
9  BEGIN
10     PROCESS
11     BEGIN
12         WAIT UNTIL Clock'EVENT AND Clock = '1' ;
13         IF L = '1' THEN
14             Q <= R ;
15         ELSE
16             Q(0) <= Q(1) ;
17             Q(1) <= Q(2) ;
18             Q(2) <= Q(3) ;
19             Q(3) <= w ;
20         END IF ;
21     END PROCESS ;
22 END Behavior ;
```

BUFFER mode allows Q to appear on both the left and right sides of signal assignments

A WAIT UNTIL statement implies all signals assigned a value inside the process have to be implemented as the output of a flip-flop

Identical code, which reverses the ordering of statements 16 – 19 in L05/S30

```
1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;

3  ENTITY shift4 IS
4      PORT ( R          : IN          STD_LOGIC_VECTOR( 3 DOWNT0 0) ;
5            L, w, Clock : IN          STD_LOGIC ;
6            Q          : BUFFER      STD_LOGIC_VECTOR( 3 DOWNT0 0) ) ;
7  END shift4;

8  ARCHITECTURE Behavior OF shift4 IS
9  BEGIN
10     PROCESS
11     BEGIN
12         WAIT UNTIL Clock'EVENT AND Clock = '1' ;
13         IF L = '1' THEN
14             Q <= R ;
15         ELSE
16             Q(3) <= w ;
17             Q(2) <= Q(3) ;
18             Q(1) <= Q(2) ;
19             Q(0) <= Q(1) ;
20         END IF ;
21     END PROCESS ;
22 END Behavior ;
```

IMPORTANT:

Why is the statement order immaterial?

Code for an n -bit left-to-right shift register

```
1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;

3  ENTITY shiftn IS
4      GENERIC ( N : INTEGER := 8 ) ;
5      PORT ( R      : IN      STD_LOGIC_VECTOR( N-1 DOWNT0 0 ) ;
6            L, w, Clock : IN      STD_LOGIC ;
7            Q      : BUFFER STD_LOGIC_VECTOR( N-1 DOWNT0 0 ) ) ;
8  END shiftn;

9  ARCHITECTURE Behavior OF shiftn IS
10 BEGIN
11     PROCESS
12     BEGIN
13         WAIT UNTIL Clock'EVENT AND Clock = '1' ;
14         IF L = '1' THEN
15             Q <= R ;
16         ELSE
17             Genbits: FOR i IN 0 to N-2 LOOP
18                 Q(i) <= Q(i+1) ;
19             END LOOP ;
20             Q(N-1) <= w ;
21         END IF ;
22     END PROCESS ;
23 END Behavior ;
```


Just as the FOR GENERATE statement is used to generate a set of concurrent statements, the FOR LOOP statement is used to generate a set of sequential statements

Flip-flop timing parameters

- Three important parameters that need to be considered in the design of sequential circuits:
 - *Propagation delay*, t_{cQ} , the time needed for the output of the FF to change after the triggering clock edge has occurred
 - *Setup time*, t_{su} , the time interval the input needs to be stable for prior to the triggering clock edge, for it to be reliably read
 - *Hold time*, t_h , the time interval the input needs to be stable for after the triggering clock edge, for it to be reliably read
- The magnitude of these parameters depend upon the design of the flip-flop, the process technology used to implement them, and the source voltage


Propagation delay

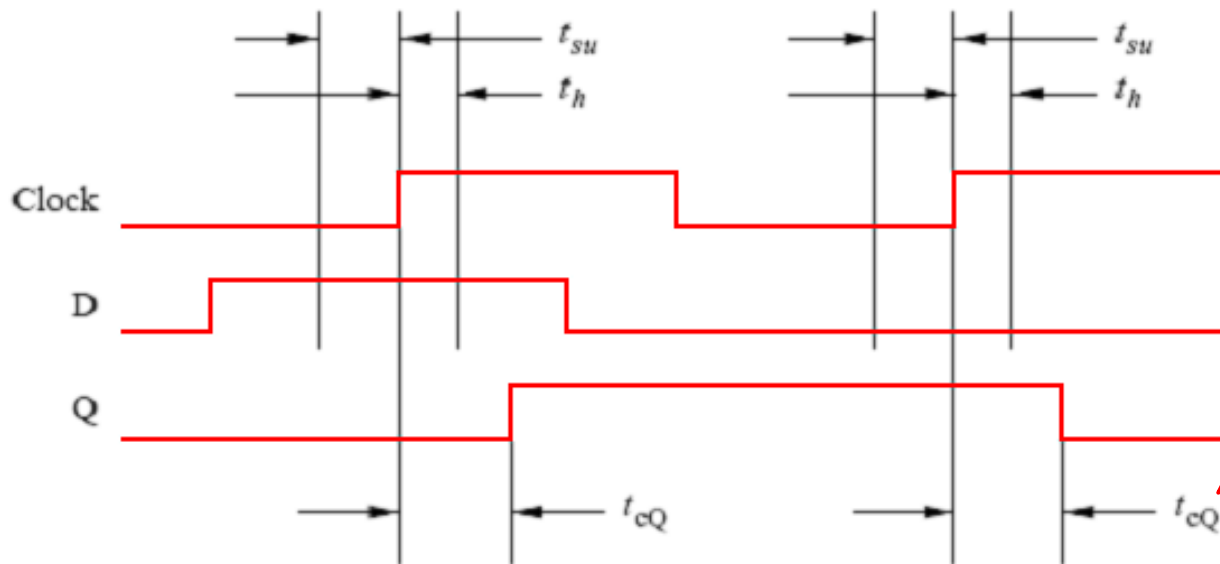- Propagation delay is the time it takes for the new value to emerge from a flip-flop after the triggering edge*




t_{cQ} (propagation delay) may not be the same for $0 \rightarrow 1$ and $1 \rightarrow 0$ transitions, and is usually specified using min and max values

t_{cQ} for a gated D latch

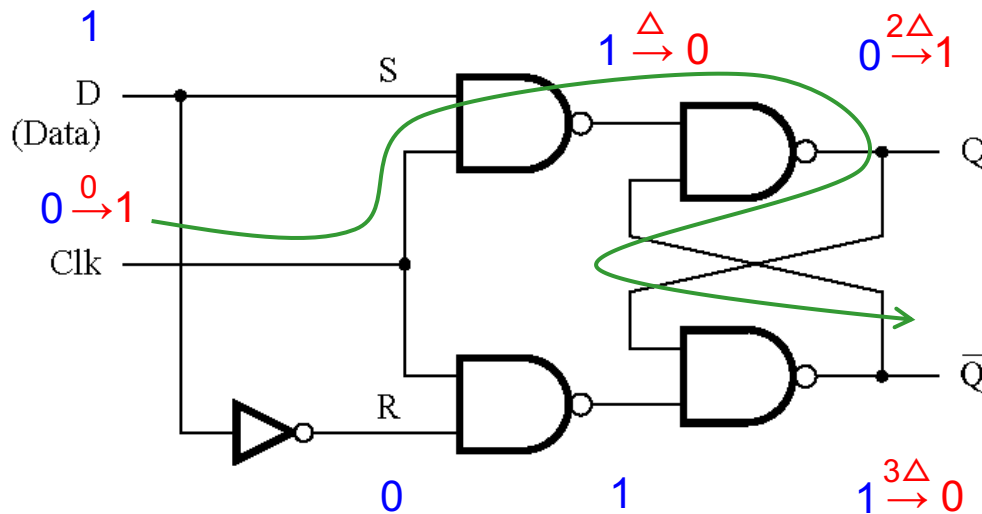


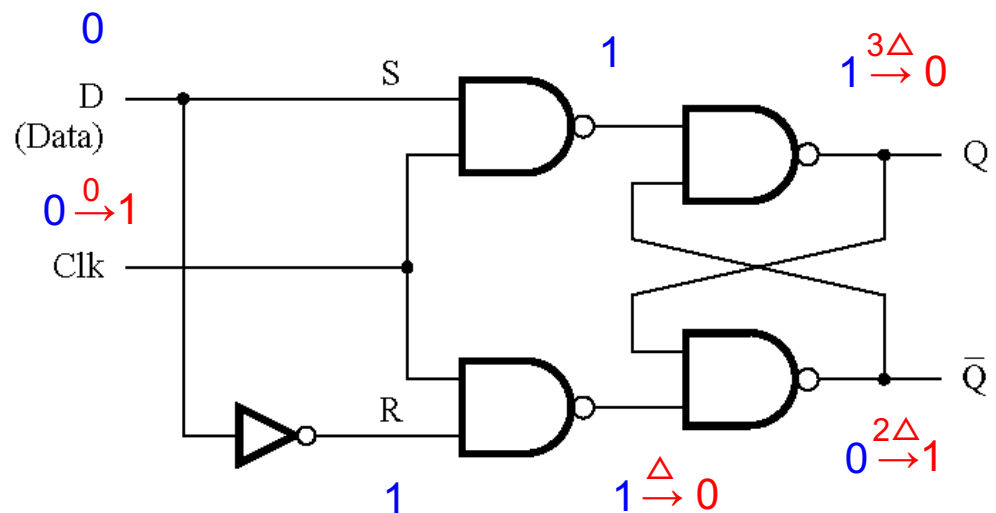Here, t_{cQ} is 2Δ for 0 → 1 transitions, but 3Δ for 1 → 0 transitions




Setup and hold times

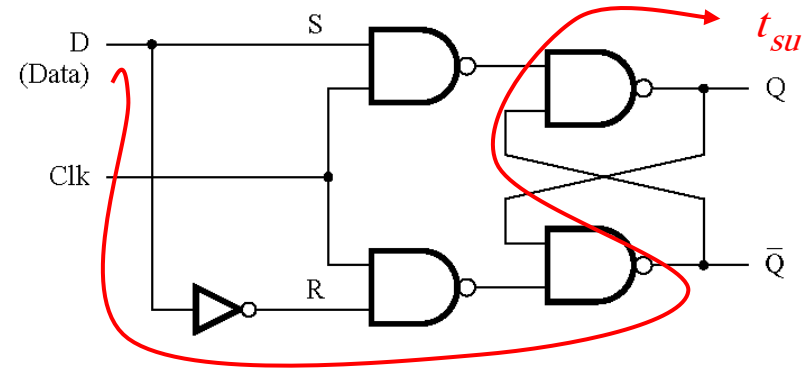- The designer of the circuit that generates the D signal must ensure setup and hold times are satisfied
- Together, they define a window of time around the triggering clock edge during which D must be stable
- Typical values for 28nm CMOS are $t_{su} = 0.03 \text{ ns}$ and $t_h = 0.02 \text{ ns}$




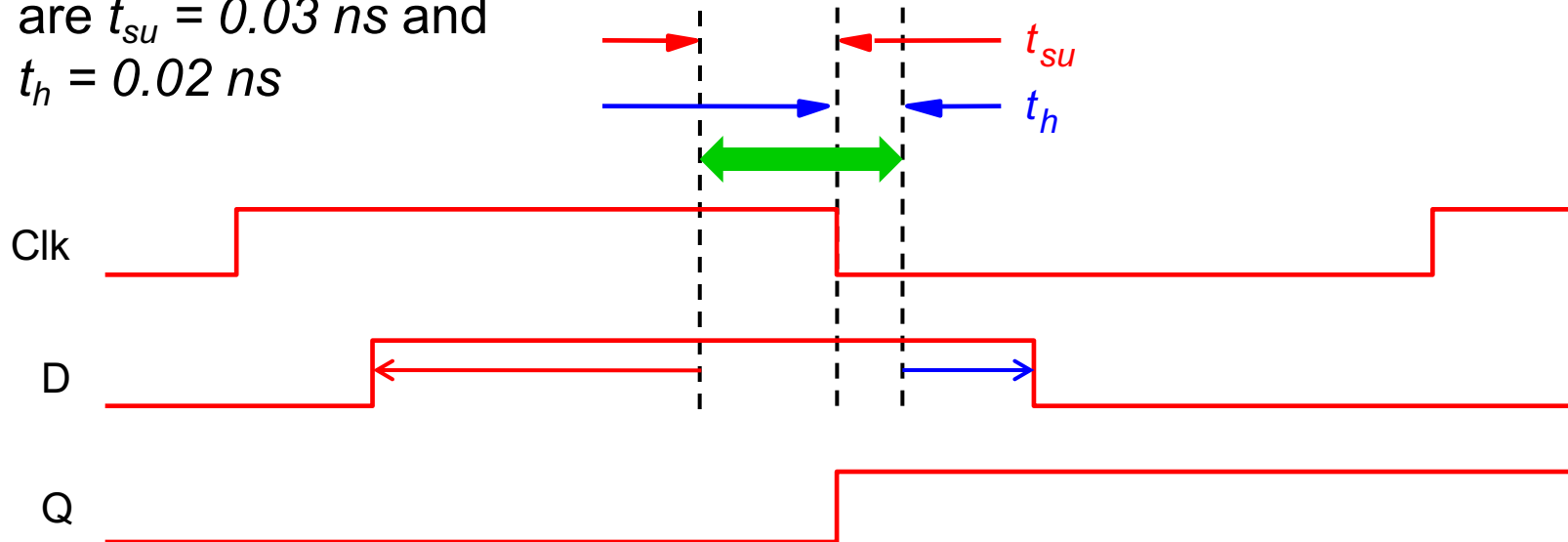(a) Circuit



$t_{su} \Rightarrow$ a change in D has to have had time to be seen at the outputs before the negative Clk edge



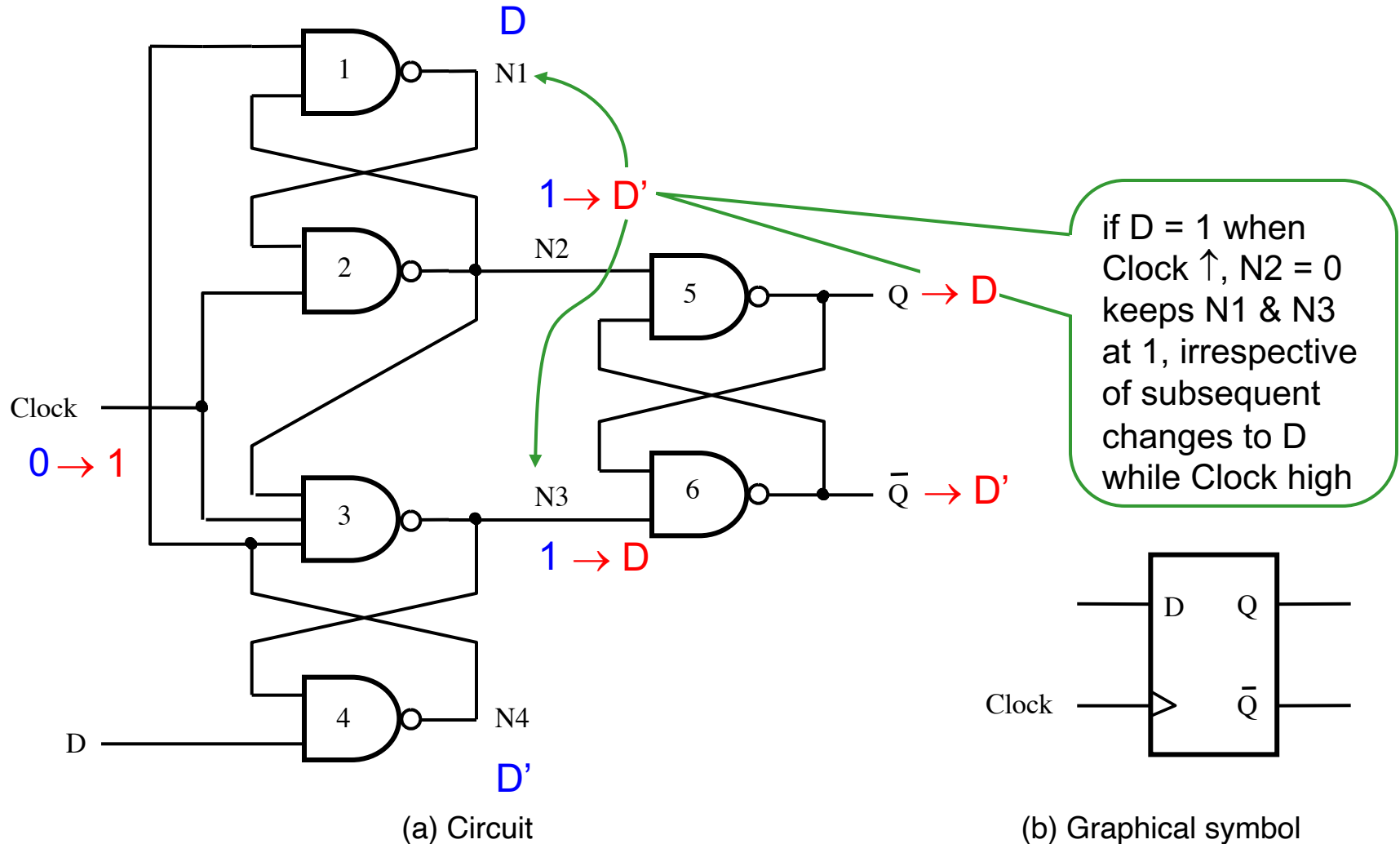
Recall positive-edge-triggered D flip-flop



  t_h for a positive-edge-triggered D flip-flop




(a) Normal operation

 

(b) Hold time violation

The larger ϵ is, the less likely it is for N2 to be held high

T flip-flop


 


T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

(b) Characteristic table

  
(c) Characteristic equation:

$$Q(t+1) = T \cdot Q'(t) + T' \cdot Q(t) \\ = T \text{ XOR } Q(t)$$



JK flip-flop

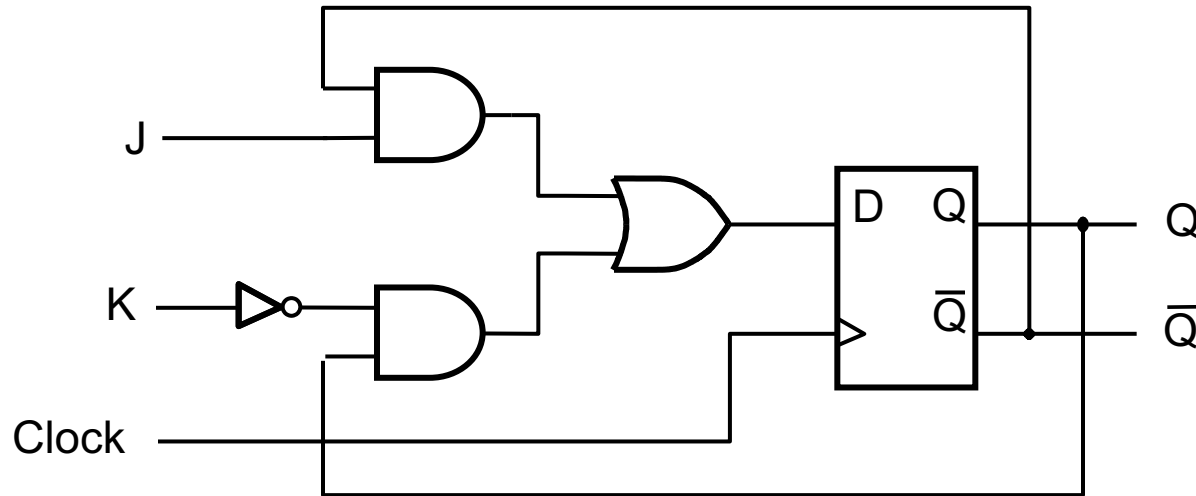
- Combines the features of an SR flip-flop and a T flip-flop



(a) Circuit

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

(b) Characteristic table

 


(c) Graphical symbol


A three-bit up-counter (ripple counter)

T	$Q(t+1)$
0	$Q(t)$
1	$\overline{Q}(t)$



Characteristic table

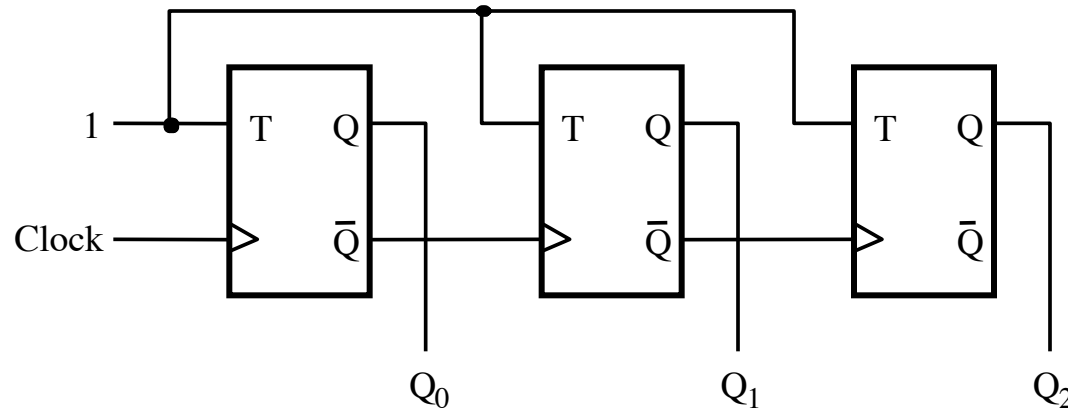

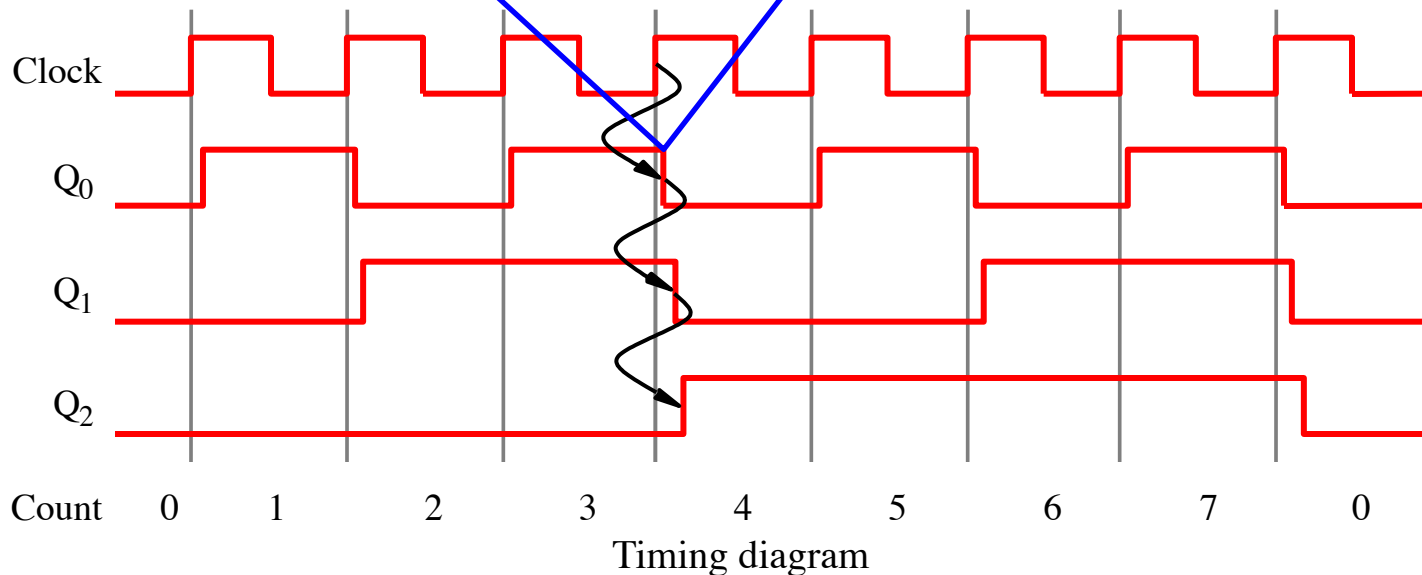The ripple effect of the triggering edge due to t_{cQ} propagation delays causes glitching from 011 \rightarrow 010 \rightarrow 000 \rightarrow 100



A three-bit down-counter

  


Timing diagram

Derivation of a synchronous up-counter

(based on T flip-flops triggered by the one clock signal) in which all output bits change at the same time

Clock cycle	Q ₂	Q ₁	Q ₀
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

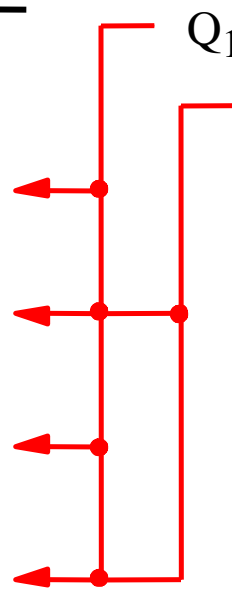

Q₁ changes

Q₂ changes

$$T_0 = 1$$

$$T_1 = Q_0$$

$$T_2 = Q_0 Q_1$$



$$T_3 = Q_0 Q_1 Q_2$$

...

$$T_n = Q_0 Q_1 \dots Q_{n-1}$$


A four-bit synchronous up-counter

 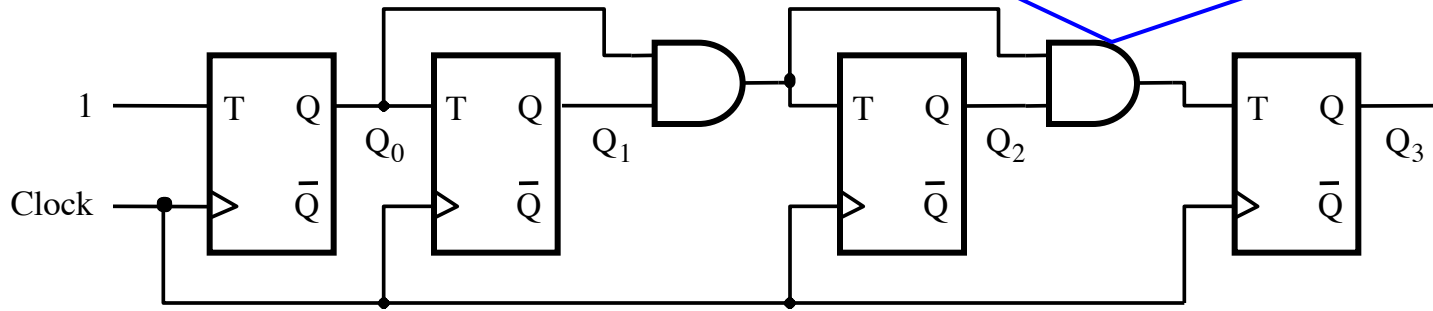Need to ensure that the $clock_period \geq t_{cQ} + \text{delay of the AND gate chain} + t_{su}$





Timing diagram

 Inclusion of an Enable and asynchronous Clear capability



 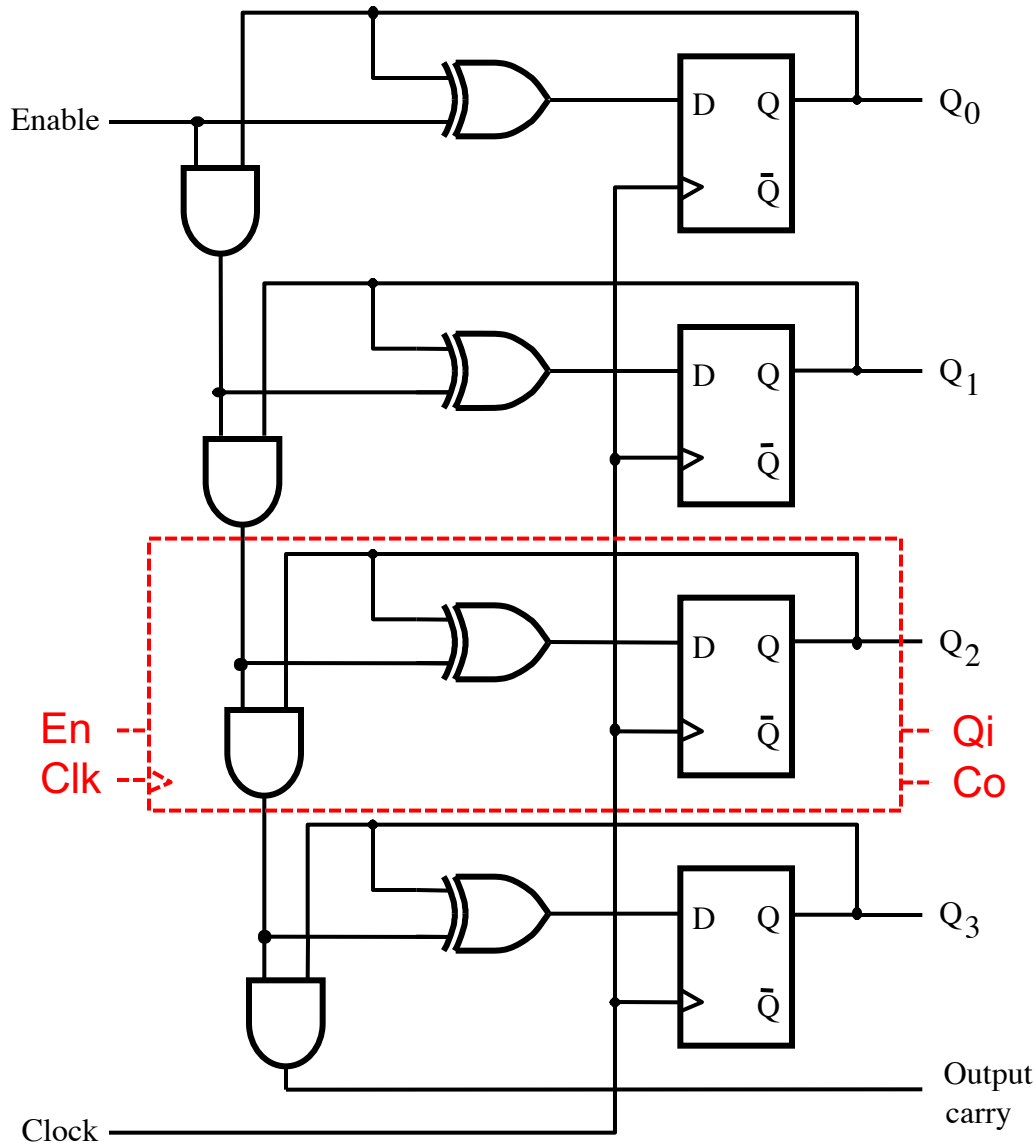A four-bit synchronous counter with D FFs



T flip-flop:
 $Q(t+1) = T \text{ XOR } Q(t)$

Can you see how you would describe the structure in VHDL?

Behavioural code for a four-bit up-counter with asynchronous clear

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE ieee.std_logic_unsigned.all ;
```

Needed to be able
to increment Count

```
ENTITY upcount IS  
    PORT (    Clock, Resetn, E : IN          STD_LOGIC ;  
            Q                : OUT         STD_LOGIC_VECTOR( 3 DOWNT0 0 ) ) ;  
END upcount;
```


```
ARCHITECTURE Behavior OF upcount IS  
    SIGNAL Count : STD_LOGIC_VECTOR( 3 DOWNT0 0 ) ;  
BEGIN  
    PROCESS (Clock, Resetn )  
    BEGIN  
        IF Resetn = '0' THEN  
            Count <= "0000" ;  
        ELSIF (Clock'EVENT AND Clock = '1') THEN  
            IF E = '1' THEN  
                Count <= Count + 1 ;  
            ELSE  
                Count <= Count ;  
            END IF ;  
        END IF ;  
    END PROCESS ;  
    Q <= Count ;  
END Behavior ;
```

Advantages of behavioural
code over structural code for
this design?

While not required
because of implied
memory semantics,
this statement is
included for clarity

Starting the count from any value

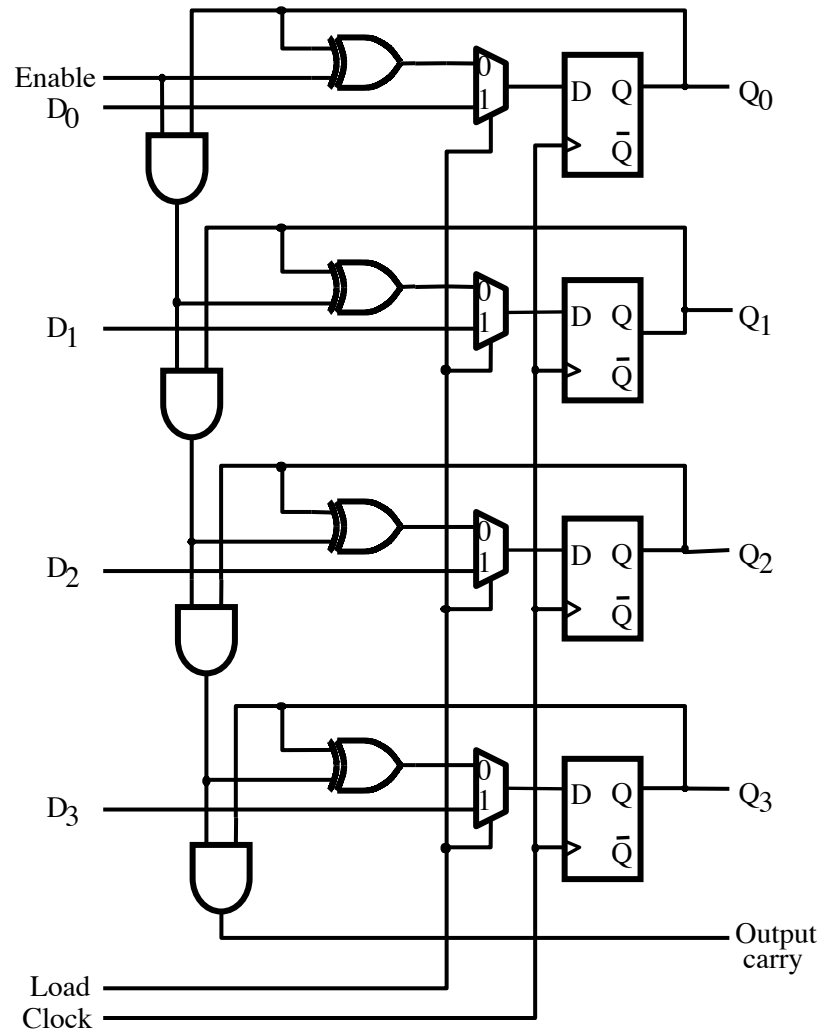- A counter with parallel-load capability



A four-bit counter with parallel load, using INTEGER signals


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY upcount IS
    PORT (    R                : IN          INTEGER RANGE 0 TO 15 ;
            Clock, Resetn, L : IN          STD_LOGIC ;
            Q                : BUFFER       INTEGER RANGE 0 TO 15 ) ;
END upcount;

ARCHITECTURE Behavior OF upcount IS
BEGIN
    PROCESS (Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN
            Q <= 0 ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF L = '1' THEN
                Q <= R ;
            ELSE
                Q <= Q + 1 ;
            END IF;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Controlling the count range

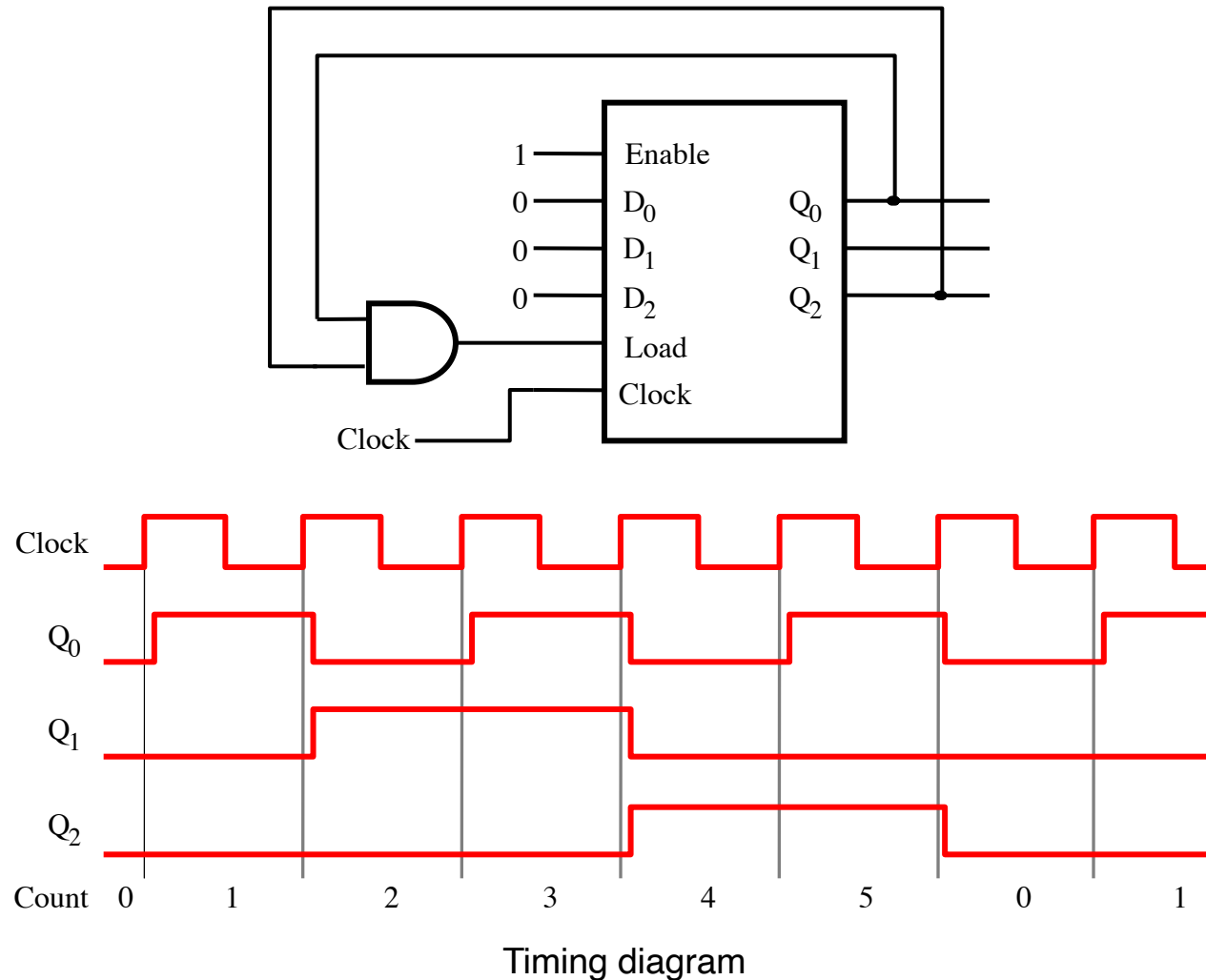- A modulo-6 counter with synchronous reset





Code for a down-counter

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY downcnt IS
    GENERIC ( modulus          : INTEGER := 8 ) ;
    PORT (   Clock, L, E      : IN          STD_LOGIC ;
            Q                  : OUT        INTEGER RANGE 0 TO modulus-1 ) ;
END downcnt;


ARCHITECTURE Behavior OF downcnt IS
    SIGNAL Count : INTEGER RANGE 0 TO modulus-1 ;
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL (Clock'EVENT AND Clock = '1') ;
        IF L = '1' THEN
            Count <= modulus-1 ;
        ELSE
            IF E = '1' THEN
                Count <= Count-1 ;
            END IF;
        END IF ;
    END PROCESS ;
    Q <= Count ;
END Behavior ;
```

  A modulo-6 counter with asynchronous reset




Glitching is undesirable: can have unintended consequences if not designed away from the outset


A two-digit BCD counter

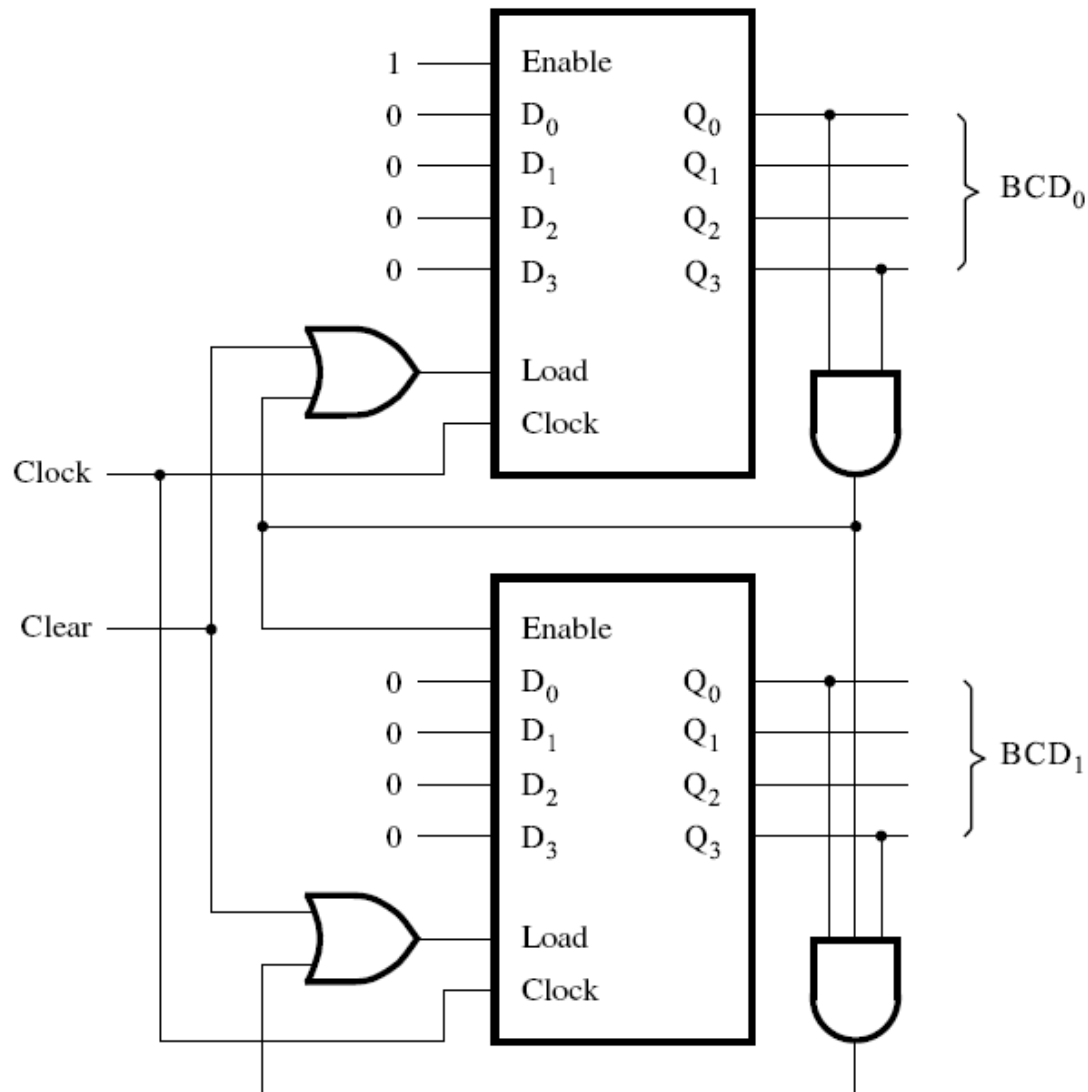

Ring counter

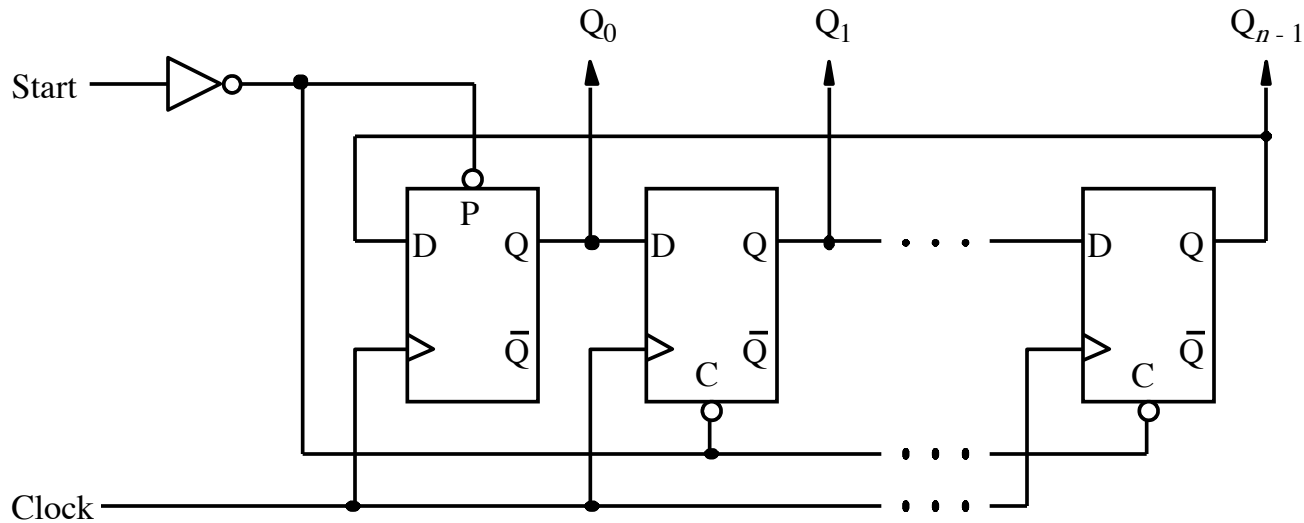

(a) An n -bit ring counter

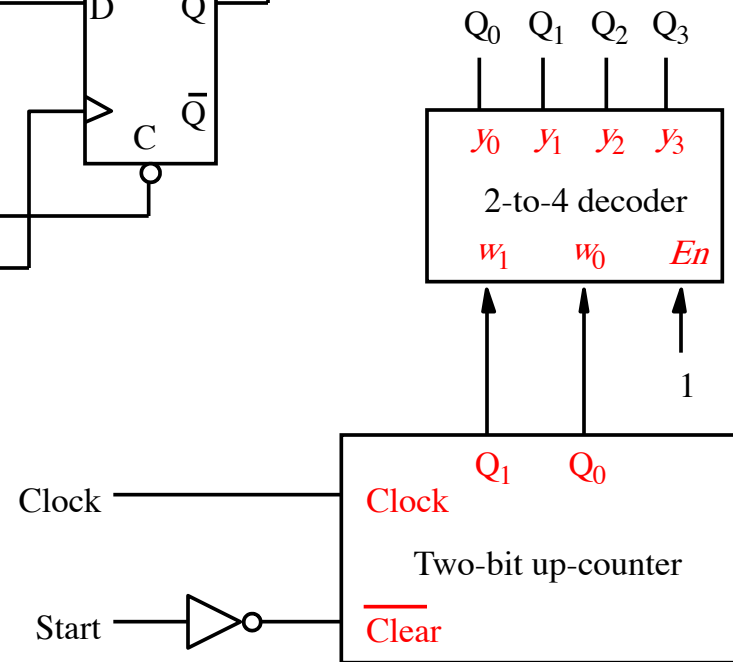

(b) A four-bit ring counter


Timing analysis of flip-flop circuits

- Usually the maximum clock frequency a circuit can be operated at, F_{max} , needs to be determined
- Whether any hold times are violated also needs to be determined
- Timing parameters of flip-flops were introduced in slides L05/S33 to L05/S38 – these include the set-up time t_{su} , the hold time t_h , and the clock-to-Q propagation delay t_{cQ}

Timing analysis of a simple flip-flop circuit

- Consider the simple circuit shown, and let's assume that $t_{su} = 0.6$ ns, $t_h = 0.4$ ns, and 0.8 ns $\leq t_{cQ} \leq 1.0$ ns
- Furthermore, assume the delay of a k -input gate is $1 + 0.1k$ ns
- To calculate $T_{min} = 1/F_{max}$, we need to determine the longest timing path in the circuit (a.k.a. *critical path*) that starts and ends at a flip-flop
- Here:
$$T_{min} = \max\{t_{cQ}\} + t_{NOT} + t_{su}$$
$$\text{i.e. } T_{min} = 1.0 + 1.1 + 0.6 = 2.7 \text{ ns}$$
$$\text{and } F_{max} = 1/T_{min} = 370 \text{ MHz}$$

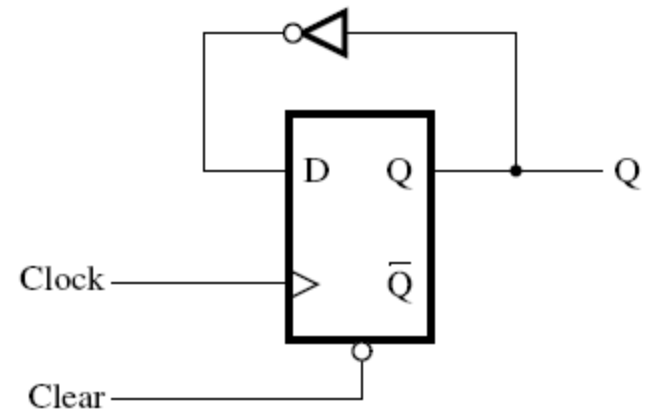any faster, and t_{su} would not be satisfied
- Need to check hold time violations by considering the shortest possible delay from any +ve clock edge to any flip-flop input
- Here:
$$\min\{t_{cQ}\} + t_{NOT} = 0.8 + 1.1 = 1.9 \text{ ns}$$
$$> t_h = 0.4 \text{ ns} \therefore \text{no violation}$$




Timing analysis of a 4-bit counter

Assume the same timing parameters as in the previous example; critical path:

$$\begin{aligned} T_{min} &= \max\{t_{cQ(Q0)}\} + 3(t_{AND}) + t_{XOR} \\ &\quad + t_{su(Q3)} \\ &= 1.0 + 3(1.2) + 1.2 + 0.6 \\ &= 6.4 \text{ ns} \end{aligned}$$

$F_{max} = 1/6.4 \text{ ns} = 156 \text{ MHz}$
(this assumes Enable is well behaved; if not, F_{max} may need to be reduced)

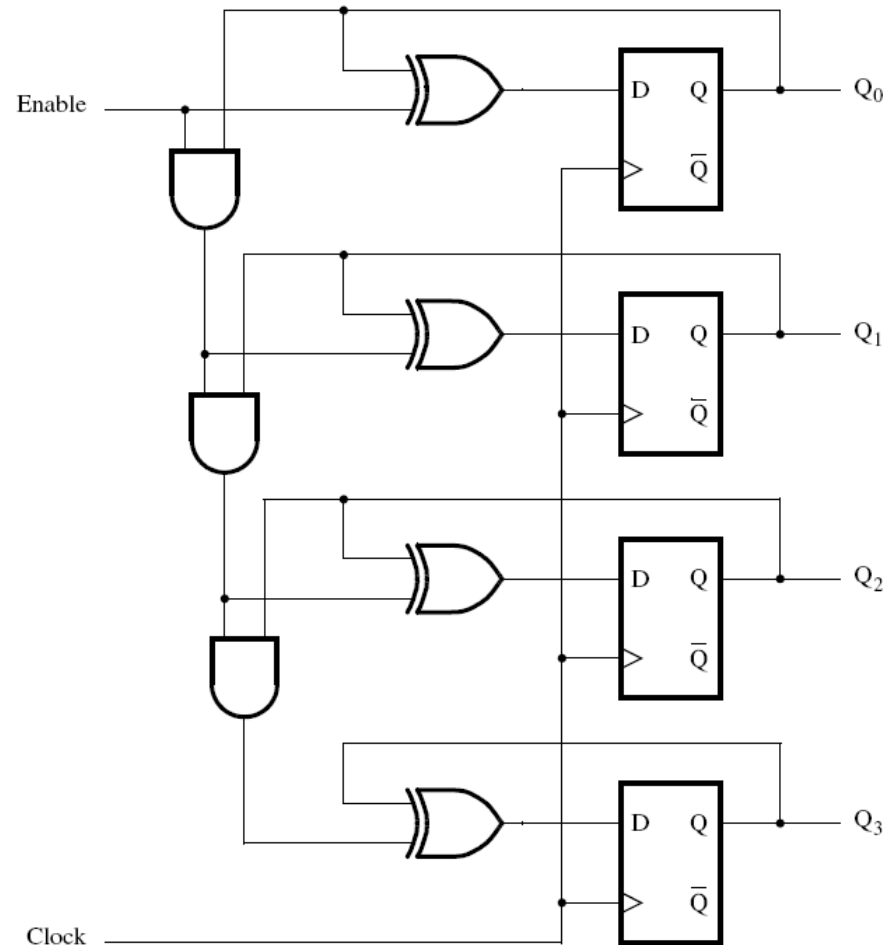Shortest path from clock to D for each FF is $\min\{t_{cQ}\} + t_{XOR} = 0.8 + 1.2 = 2.0 \text{ ns} > t_h = 0.4 \text{ ns} \therefore$
no hold violations (given Enable is well behaved)




Q: When is it best to (de)assert *Enable*?


Clock skew

- Clock skew is the spread in time (relative delay) in clock edges arriving at the various synchronous components of a digital circuit
- Mostly, these are caused by wire delays
- FPGAs have special clock distribution networks, which use low-resistance (fat) wiring tracks, buffers that amplify the clock signal, and “balanced” layouts, such as H-trees with the root located at the centre of the chip, to minimize clock skew

Effect of clock skew on F_{max}

 

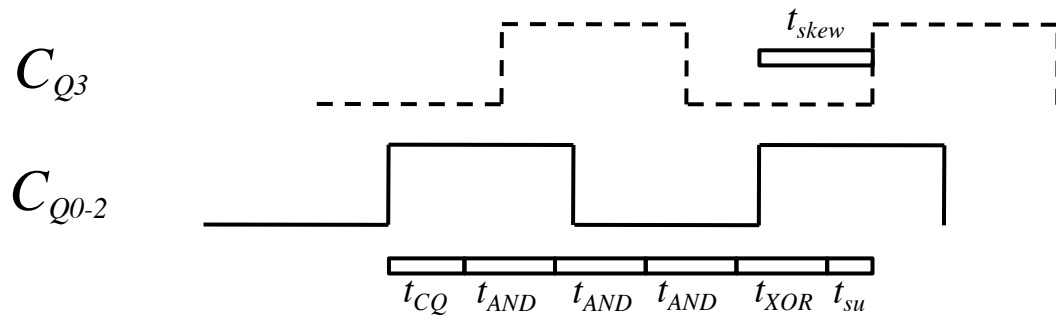
- Assume $t_{skew} = 1.5ns$ delay on clock pulses arriving at Q3



- Delay on path from Q0 to Q3 is then given by

$$t_{CQ} + 3(t_{AND}) + t_{XOR} + t_{su} - t_{skew} = 6.4 - 1.5 = 4.9ns$$

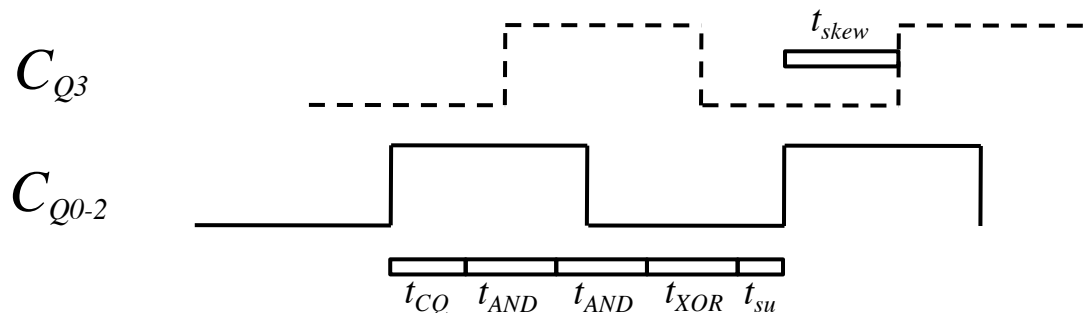since the skew provides additional time before data is loaded into Q3



- However, critical path is now from Q0 to Q2, i.e.

$$\begin{aligned} T_{min} &= t_{CQ} + 2(t_{AND}) + t_{XOR} + t_{su} \\ &= 1.0 + 2(1.2) + 1.2 + 0.6 \\ &= 5.2 ns \end{aligned}$$

$$F_{max} = 192 MHz$$

Negative clock skew

- A negative clock skew, i.e. clock arriving earlier at Q3 than at Q0 – Q2 would have the opposite effect of lengthening the clock period requirement & reducing clock frequency

Effect of clock skew on hold times

- As positive clock skew has the effect of delaying the loading of data into FF Q3, it has the effect of increasing the hold time requirement of this FF to $t_h + t_{skew}$ for all paths that end at Q3
- The shortest such path is from FF Q2 to Q3 and has delay $t_{cQ} + t_{AND} + t_{XOR} = 0.8 + 1.2 + 1.2 = 3.2 \text{ ns} > t_h + t_{skew} = 1.9 \text{ ns} \therefore$ no violation
- But, when $t_{skew} \geq 3.2 - t_h = 2.8 \text{ ns}$, then hold time violations will exist and the circuit will not work reliably at any frequency
- Good circuit design therefore aims to minimize, if not eliminate, clock skew