

# **COMP3222/9222 Digital Circuits & Systems**


## **4. Combinational Building Blocks**

# Objectives

- Learn about commonly used combinational sub-circuits
  - Multiplexers, used for signal selection and implementing general logic functions
  - Encoders, decoders and code converters
- Learn about the key VHDL constructs used to specify combinational circuits
  - Non-simple, concurrent assignment statements
  - Sequential statements
 
# Multiplexers


- A multiplexer (MUX) has a number of data inputs, one or more select inputs, and one output
  - It passes the signal value on one of the data inputs to the output
  - The data input is selected by the values of the select inputs
- A 2-to-1 MUX, which has 2 data inputs and therefore 1 select input, is shown below
  - This 2-to-1 MUX implements the function  $f = \overline{s} \cdot w_0 + s \cdot w_1$




$s$	$w_0$	$w_1$	$f$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$s$	$f$
0	$w_0$
1	$w_1$

(b) Truth table

 


# A 4-to-1 multiplexer

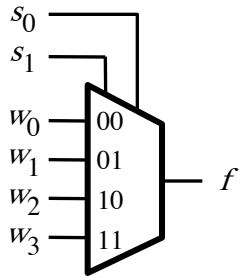

(a) Graphic symbol

$s_1$	$s_0$	$f$
0	0	$w_0$
0	1	$w_1$
1	0	$w_2$
1	1	$w_3$

(b) Truth table

 


(c) Circuit

- A 4-to-1 MUX, which has 4 data and 2 select inputs, realizes the function

$$f = \overline{s_1}\overline{s_0}w_0 + \overline{s_1}s_0w_1 + s_1\overline{s_0}w_2 + s_1s_0w_3$$


- Larger MUXes can be built using the same approach, but can also be built from smaller MUXes
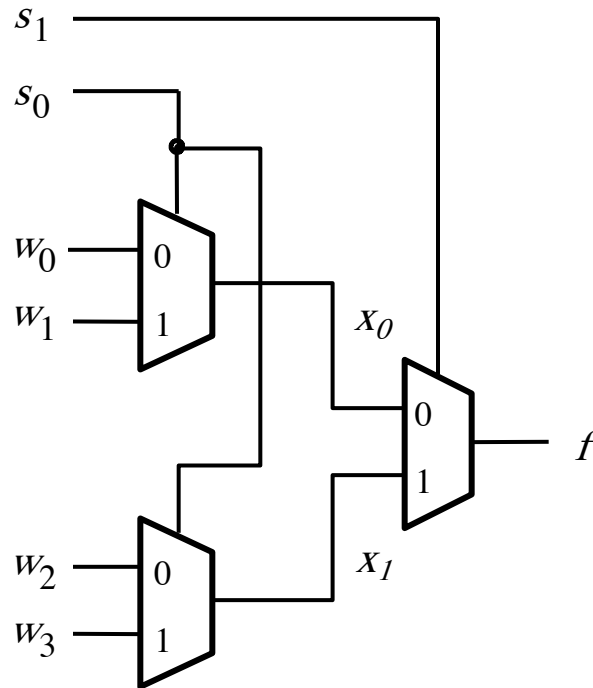
# Using 2-to-1 MUXes to build a 4-to-1 MUX



$$\begin{aligned} f &= \overline{s_1}x_0 + s_1x_1 \\ &= \overline{s_1}(\overline{s_0}w_0 + s_0w_1) + s_1(\overline{s_0}w_2 + s_0w_3) \\ &= \overline{s_1}\overline{s_0}w_0 + \overline{s_1}s_0w_1 + s_1\overline{s_0}w_2 + s_1s_0w_3 \end{aligned}$$

 
# A 16-to-1 multiplexer built from 4-to-1 MUXes




Note: from now on let us assume that the inputs selected by the MUX are numbered from 00 at the top to 11 at the bottom of the MUX symbol block
 
# Practical applications of multiplexers

- A circuit that has  $n$  inputs and  $k$  outputs, whose function it is to provide a capability to connect any input to any output, is referred to as an  $n \times k$  **crossbar switch**
- A  $2 \times 2$  crossbar switch can easily be built using two 2-to-1 multiplexers




(a) A 2x2 crossbar switch

 


(b) Implementation using multiplexers

 
# Implementing programmable switches in an FPGA



(a) Part of the FPGA in Figure 3.39

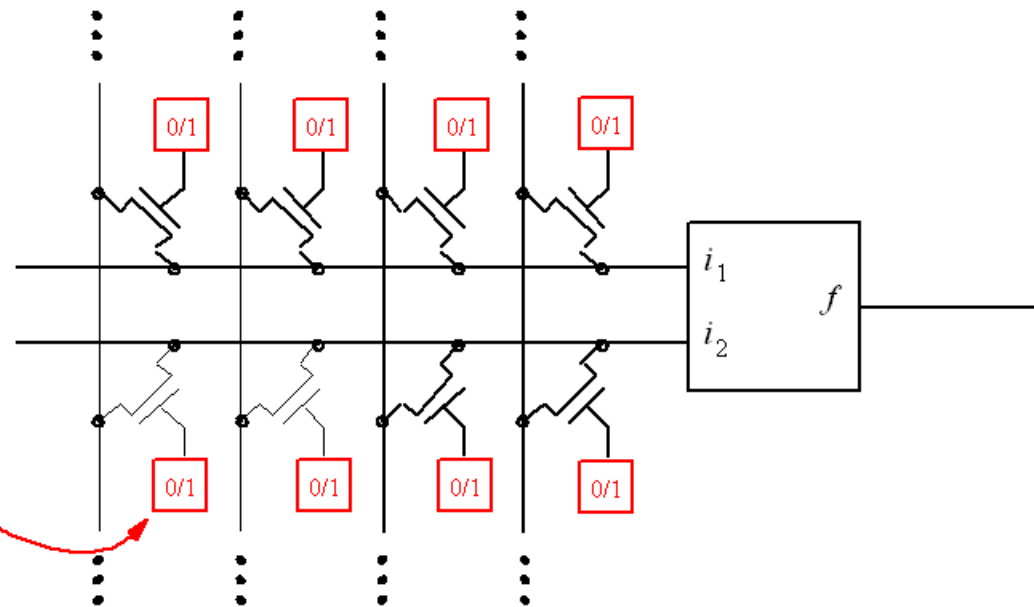

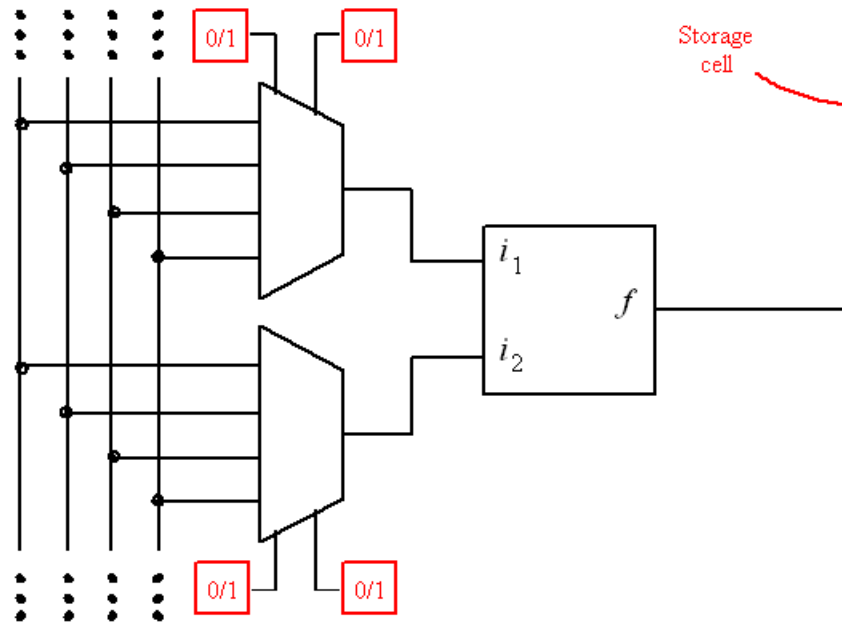(b) Implementation using pass transistors



(c) Implementation using multiplexers

Use of MUXes reduces the 6-transistor cost per storage cell and reduces the risk of creating unintended connections




# Synthesis of logic functions using multiplexers

- We can use MUXes to implement functions
- For example, consider the XOR function below
  - Each row of the truth table can be connected to a MUX input as a constant
  - The select inputs are driven by the variables of the function

- But, we can be more efficient if we rewrite the truth table:


$w_1$	$w_2$	$f$		$w_1$	$f$
0	0	0	}	0	$w_2$
0	1	1		1	$\bar{w}_2$
1	0	1	}		
1	1	0			

$w_1$	$w_2$	$f$
0	0	0
0	1	1
1	0	1
1	1	0

 

(a) Implementation using a 4-to-1 multiplexer

(b) Modified truth table

 


(c) Circuit

# 3-input majority fn using a 4-to-1 MUX

- In a similar manner, we can efficiently implement other functions

$w_1$	$w_2$	$w_3$	$f$		$w_1$	$w_2$	$f$
0	0	0	0	}	0	0	0
0	0	1	0		0	1	$w_3$
0	1	0	0	}	1	0	$w_3$
0	1	1	1		1	1	1
1	0	0	0	}			
1	0	1	1				
1	1	0	1	}			
1	1	1	1				

(a) Modified truth table

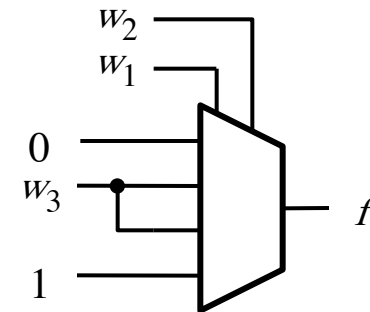

(b) Circuit

- Note that any variable pair could be used as the selector inputs without changing the circuit structure


# 3-input XOR implemented using 2-to-1 MUXes

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Red annotations in the original image:

- A red bracket groups the first four rows (where  $w_1=0$ ). To its right is the red text  $w_2 \oplus w_3$ .
- A red bracket groups the last four rows (where  $w_1=1$ ). To its right is the red text  $\overline{w_2 \oplus w_3}$ .

(a) Truth table

 


(b) Circuit

# 3-input XOR implemented with a 4-to-1 MUX

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(a) Truth table

 

(b) Circuit

# Multiplexer synthesis using Shannon's expansion

- So far, we have seen how truth tables can be interpreted to implement logic functions using MUXes
  - In each case the MUX inputs are the constant 0 & 1, or some variable or its complement
- Besides using simple inputs, it is possible to connect more complex circuits as inputs to a MUX, allowing fns to be synthesized using a combination of MUXes and other logic gates
- The next example illustrates this approach using the 3-input majority function


# 3-input majority fn implemented using a 2-to-1 MUX

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$w_1$	$f$
0	$w_2 w_3$
1	$w_2 + w_3$

(b) Truth table

 

(b) Circuit

This implementation has been derived as follows:

$$\begin{aligned}
 f &= \bar{w}_1 w_2 w_3 + w_1 \bar{w}_2 w_3 + w_1 w_2 \bar{w}_3 + w_1 w_2 w_3 \\
 &= \bar{w}_1 (w_2 w_3) + w_1 (\bar{w}_2 w_3 + w_2 \bar{w}_3 + w_2 w_3) \\
 &= \bar{w}_1 (w_2 w_3) + w_1 (w_2 + w_3)
 \end{aligned}$$

# Shannon's expansion theorem

- MUX implementations of logic fns require that a given fn be decomposed with respect to the variables that are used as the select inputs
- This can be achieved by means of Shannon's expansion theorem:

- Any Boolean function  $f(w_1, \dots, w_n)$  can be written in the form

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

(The expansion can be done w.r.t. any of the  $n$  variables.)

- Examples:

- The 3-input majority function:

$$f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$$

$$= \bar{w}_1(w_2 w_3) + w_1(w_2 + w_3 + w_2 w_3) = \bar{w}_1(w_2 w_3) + w_1(w_2 + w_3)$$

- The 3-input XOR function:

$$\begin{aligned} f &= w_1 \oplus w_2 \oplus w_3 = \bar{w}_1(\bar{w}_2 w_3 + w_2 \bar{w}_3) + w_1(\bar{w}_2 \bar{w}_3 + w_2 w_3) \\ &= \bar{w}_1 \cdot (w_2 \oplus w_3) + w_1 \cdot (w_2 \oplus w_3) \end{aligned}$$

Residual factors of terms

that include  $\bar{w}_1$

Residual factors of terms that include  $w_1$

# Cofactors of $f$

- In Shannon's expansion, the term  $f(0, w_2, \dots, w_n)$  is called the *cofactor of  $f$*  with respect to  $\overline{w}_1$  and is denoted  $f_{\overline{w}_1}$
- Similarly, the term  $f(1, w_2, \dots, w_n)$  is called the *cofactor of  $f$*  with respect to  $w_1$ , written  $f_{w_1}$

- Hence, we can write

$$f = \overline{w}_1 f_{\overline{w}_1} + w_1 f_{w_1}$$

- In general, if the expansion is done with respect to variable  $w_i$ , then  $f_{w_i}$  denotes  $f(w_1, \dots, w_{i-1}, 1, w_{i+1}, \dots, w_n)$  and  $f(w_1, \dots, w_n) = \overline{w}_i f_{\overline{w}_i} + w_i f_{w_i}$

whereby the complexity of the expression may vary, depending on which variable  $w_i$  is used



# Complexity of cofactors

- For the function  $f = \bar{w}_1 w_3 + w_2 \bar{w}_3$ , with canonical SOP form:

$$f = \bar{w}_1 \bar{w}_2 w_3 + \bar{w}_1 w_2 w_3 + \bar{w}_1 w_2 \bar{w}_3 + w_1 w_2 \bar{w}_3,$$

decomposition using  $w_1$  gives

$$\begin{aligned} f &= \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1} \\ &= \bar{w}_1 (\bar{w}_2 w_3 + w_2 \bar{w}_3) + w_1 (w_2 \bar{w}_3) \\ &= \bar{w}_1 (w_3 + w_2) + w_1 (w_2 \bar{w}_3) \end{aligned}$$

- Using  $w_2$  instead of  $w_1$  produces

$$\begin{aligned} f &= \bar{w}_2 f_{\bar{w}_2} + w_2 f_{w_2} \\ &= \bar{w}_2 (\bar{w}_1 w_3) + w_2 (\bar{w}_1 + \bar{w}_3) \end{aligned}$$

- Finally, using  $w_3$  gives

$$\begin{aligned} f &= \bar{w}_3 f_{\bar{w}_3} + w_3 f_{w_3} \\ &= \bar{w}_3 (w_2) + w_3 (\bar{w}_1), \text{ which is clearly better} \\ &\quad \text{b/c it involves less gates} \end{aligned}$$

# Shannon's expansion with more than one variable

- Shannon's expansion can also be carried out with respect to more than one variable
- For example, expanding a function with respect to variables  $w_1$  and  $w_2$  gives

$$\begin{aligned} f(w_1, w_2, \dots, w_n) = & \bar{w}_1 \bar{w}_2 \cdot f(0, 0, w_3, \dots, w_n) + \bar{w}_1 w_2 \cdot f(0, 1, w_3, \dots, w_n) \\ & + w_1 \bar{w}_2 \cdot f(1, 0, w_3, \dots, w_n) + w_1 w_2 \cdot f(1, 1, w_3, \dots, w_n) \end{aligned}$$

which is in a form that can be implemented with a 4-to-1 MUX using  $w_1$  and  $w_2$  as the select inputs


- When an expansion is carried out with respect to all  $n$  variables, a canonical SOP form results

# Example

- Say we wish to implement  $f = \bar{w}_1\bar{w}_3 + w_1w_2 + w_1w_3$  using a 2-to-1 MUX and any other necessary gates.

- Shannon's expansion using  $w_1$  gives

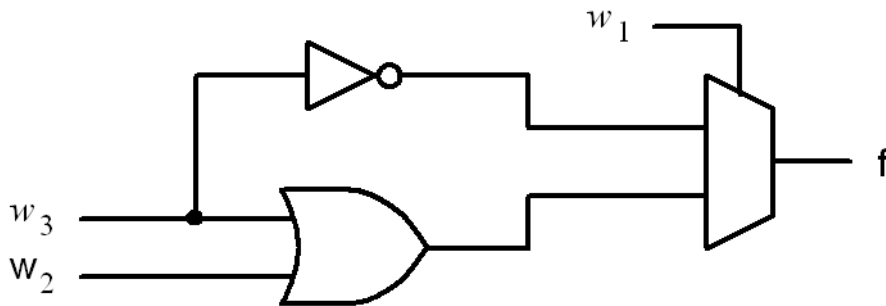
$$\begin{aligned} f &= \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1} \\ &= \bar{w}_1(\bar{w}_3) + w_1(w_2 + w_3) \end{aligned}$$



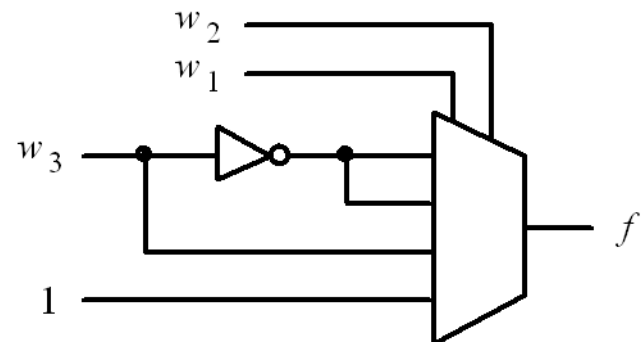(a) Using a 2-to-1 multiplexer

- If we wish to use a 4-to-1 MUX instead, we can decompose with  $w_2$  as well to give:

$$\begin{aligned} f &= \bar{w}_1\bar{w}_2 f_{\bar{w}_1\bar{w}_2} + \bar{w}_1w_2 f_{\bar{w}_1w_2} \\ &\quad + w_1\bar{w}_2 f_{w_1\bar{w}_2} + w_1w_2 f_{w_1w_2} \\ &= \bar{w}_1\bar{w}_2(\bar{w}_3) + \bar{w}_1w_2(\bar{w}_3) \\ &\quad + w_1\bar{w}_2(w_3) + w_1w_2(1) \end{aligned}$$




(b) Using a 4-to-1 multiplexer

# Example: 3-input majority function

- Consider the 3-input majority function

$$\begin{aligned} f &= w_1w_2 + w_1w_3 + w_2w_3 \\ &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3) \\ &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3) \end{aligned}$$

 - Let  $g = w_2w_3$  and  $h = w_2 + w_3$
- Expansion of both  $g$  and  $h$  with respect to  $w_2$  gives
$$g = \bar{w}_2(0) + w_2(w_3)$$
$$h = \bar{w}_2(w_3) + w_2(1)$$
- The resulting circuit is as for the 4-to-1 MUX implementation of L04/S10



# Example: mapping to 3-LUTs

- Some FPGAs may use 3-input lookup tables (3-LUTs) to implement logic functions

- Any fn of 4 variables can be mapped to at most three 3-LUTs

- Consider

$$f = \bar{w}_2 w_3 + \bar{w}_1 w_2 \bar{w}_3 + w_2 \bar{w}_3 w_4 + w_1 \bar{w}_2 \bar{w}_4$$


- Expansion with respect to  $w_1$  produces

$$f = \bar{w}_1 (\bar{w}_2 w_3 + w_2 \bar{w}_3) + w_1 (\bar{w}_2 w_3 + w_2 \bar{w}_3 w_4 + \bar{w}_2 \bar{w}_4)$$


- Using  $w_2$  instead of  $w_1$  gives

$$f = \bar{w}_2 (w_3 + w_1 \bar{w}_4) + w_2 (\bar{w}_1 \bar{w}_3 + \bar{w}_3 w_4)$$

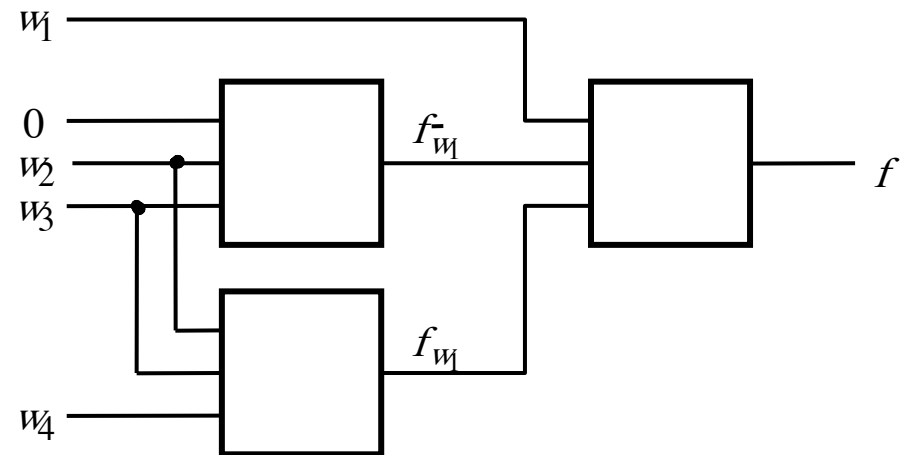Implements the truth table for any function of 3 variables



(a) Using three 3-LUTs

 


$f_{w_2} = \bar{f}_{\bar{w}_2}$  in this case

(b) Using two 3-LUTs
 
# Decoders


- Decoder circuits are used to decode encoded information
- A *binary decoder* (DEC), as shown below, is a logic circuit with  $n$  inputs and  $2^n$  outputs
- Only one output is asserted at a time, and each output corresponds to one valuation of the inputs
- The decoder also has an enable input  $En$  that is used to disable the outputs so that no output is asserted when  $En = 0$



# A 2-to-4 binary decoder


$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 

 
(b) Graphical symbol

- An n-bit binary code in which exactly one of the bits is set to 1 at a time is called *one-hot encoded*
  - The single bit that is set to 1 is said to be “hot”
- The outputs of a binary decoder are one-hot encoded
- Larger decoders can be built using the SOP structure of (c), or they can be built from smaller decoders




(c) Logic circuit
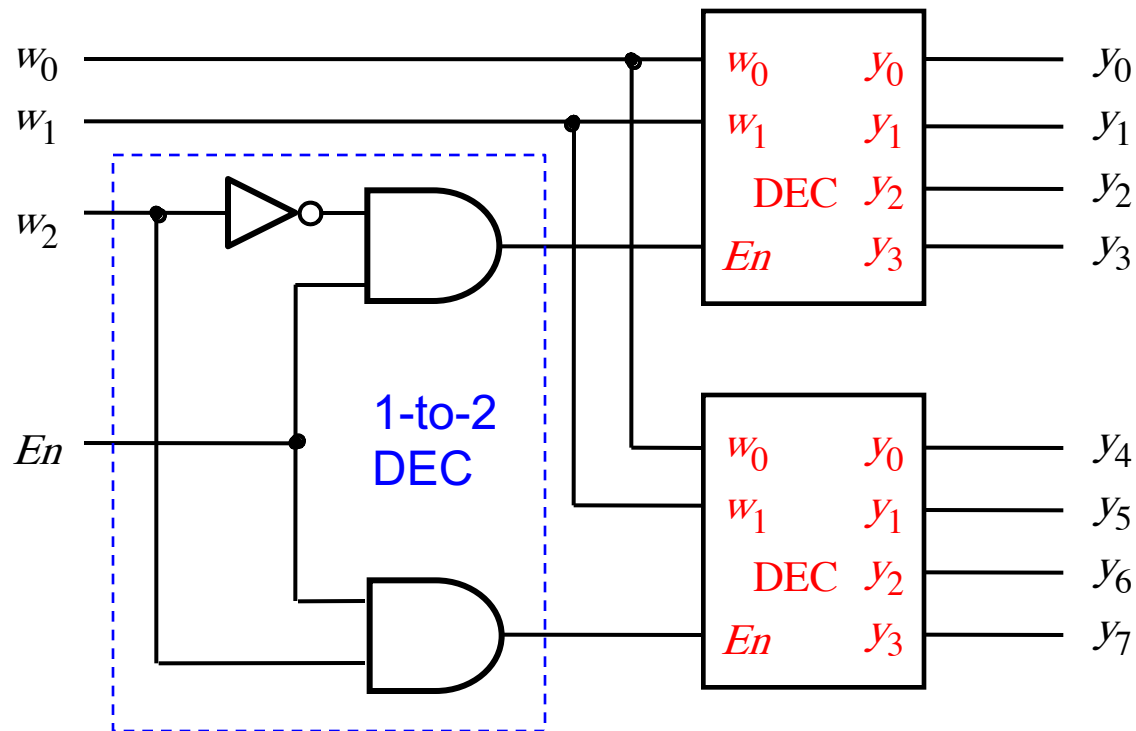
# A 3-to-8 decoder using two 2-to-4 decoders






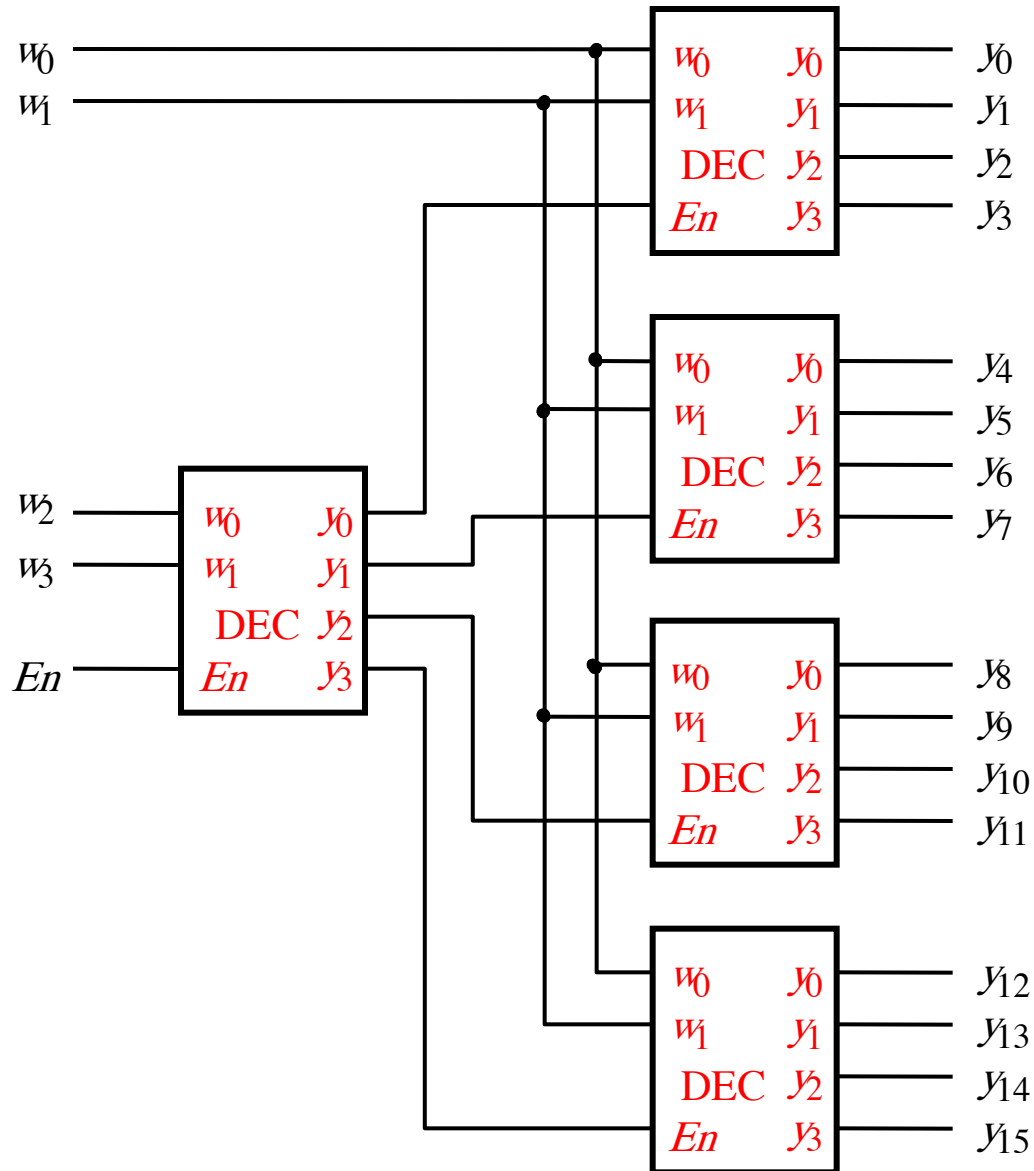
# A 4-to-16 decoder built using a decoder tree


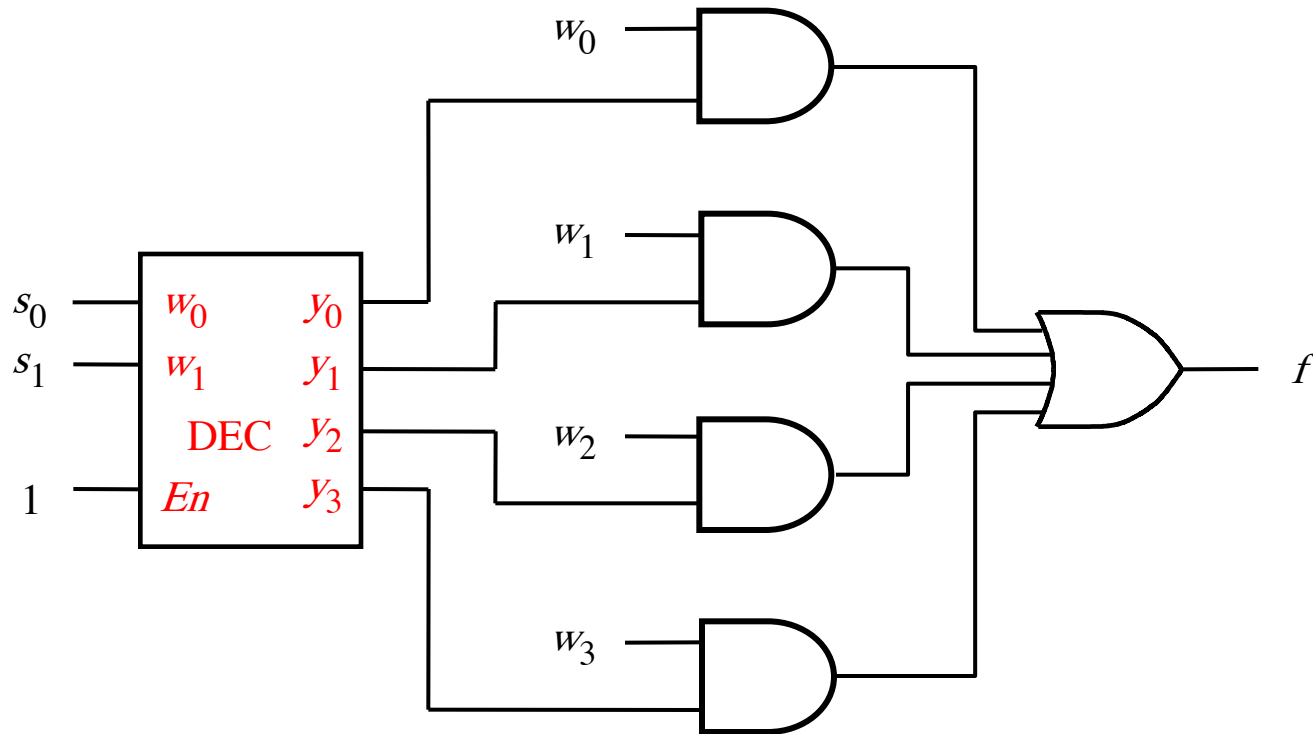
# A 4-to-1 multiplexer built using a decoder




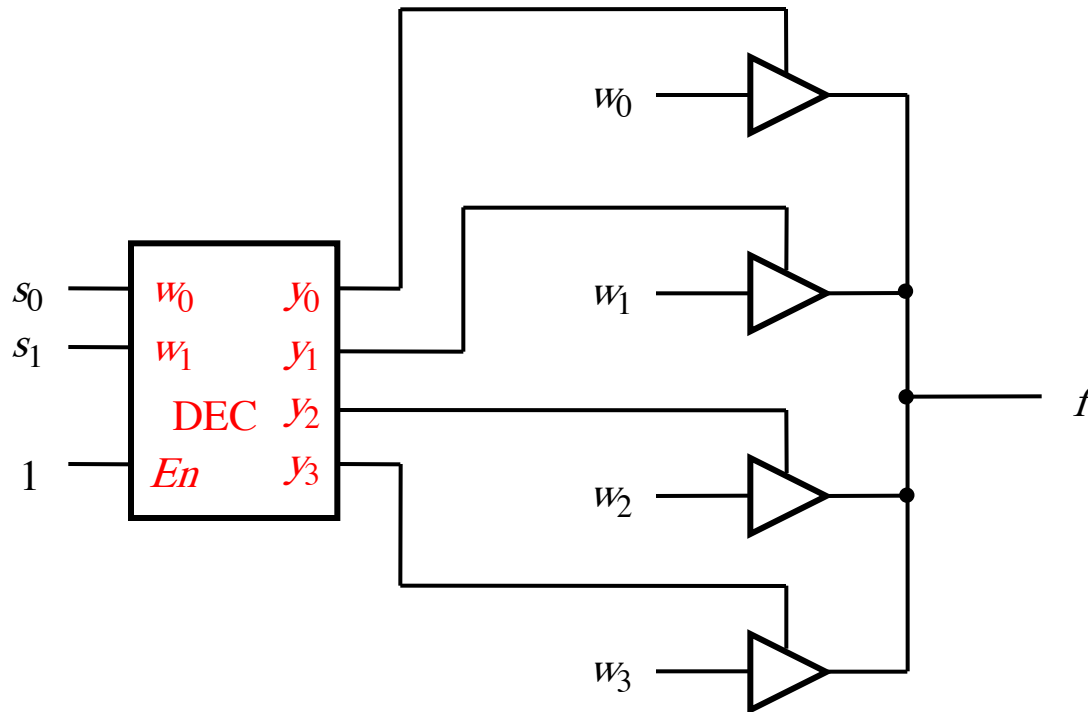
# Using a DEC & 3-state buffers to build a 4-to-1 MUX



- 3-state buffers are short-circuit when the control input is asserted, and high-impedence (high-Z  $\approx$  open circuit) when the control input is deasserted
- This allows their outputs to be tied together as long as only one buffer is asserted at a time (as ensured here by the decoder)

 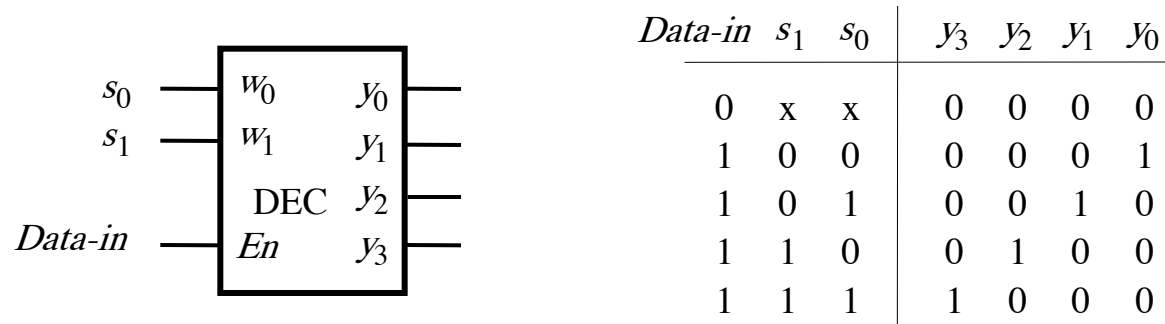
# Demultiplexing

- Note that a decoder on its own can also be used as a  $1\text{-to-}2^n$  demultiplexer
  - The  $En$  input plays the role of data-in and one of  $2^n$  outputs is selected using the  $n$  select bits



Basis for a simple *time-division multiplexed* communications system, which saves wires/channel
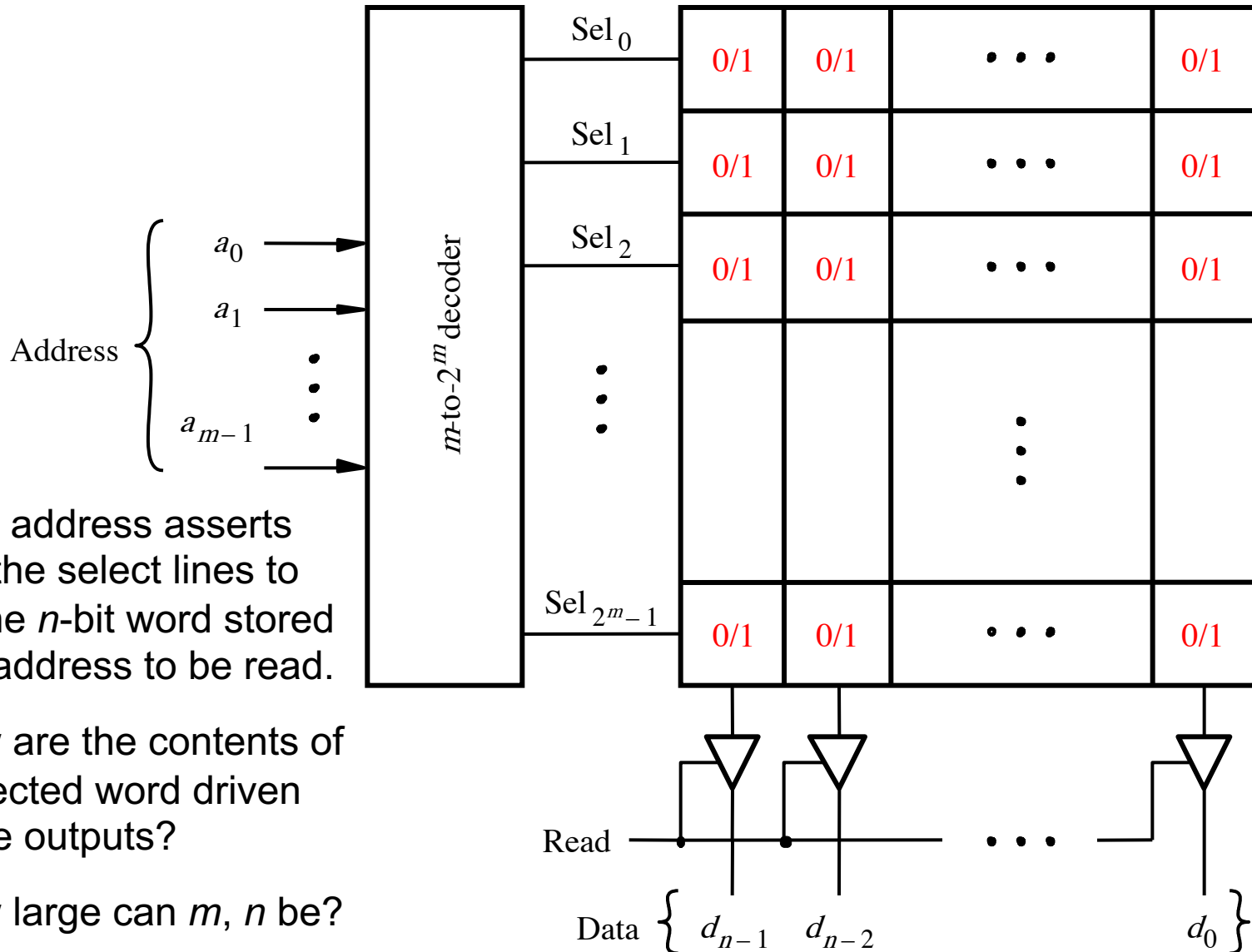
# Use of DEC block to decode address for $2^m \times n$ ROM (read-only memory) block




A given address asserts one of the select lines to allow the  $n$ -bit word stored at that address to be read.

Q: How are the contents of the selected word driven onto the outputs?

Q: How large can  $m, n$  be?
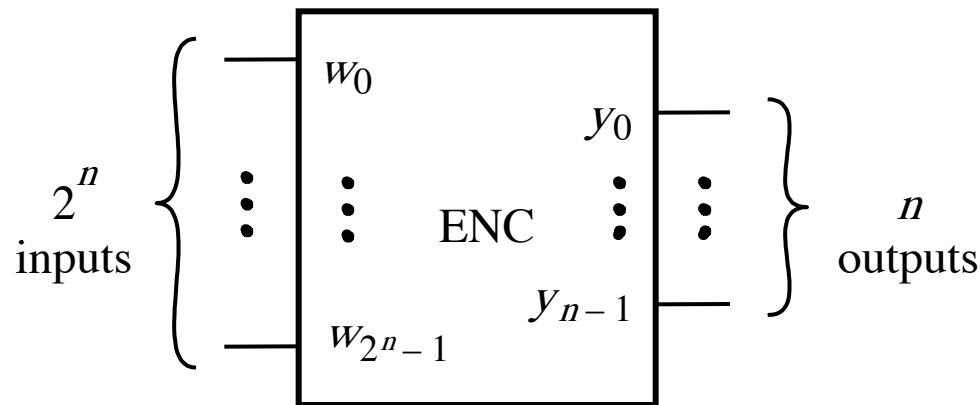
# Encoders


- An encoder performs the opposite function of a decoder
  - It encodes given information into a more compact form
- A *binary encoder* encodes information from  $2^n$  inputs into an  $n$ -bit code as shown below
- Exactly one of the input signals should have a value of 1, and the outputs present the binary number that identifies which input is equal to 1



# A 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(a) Truth table

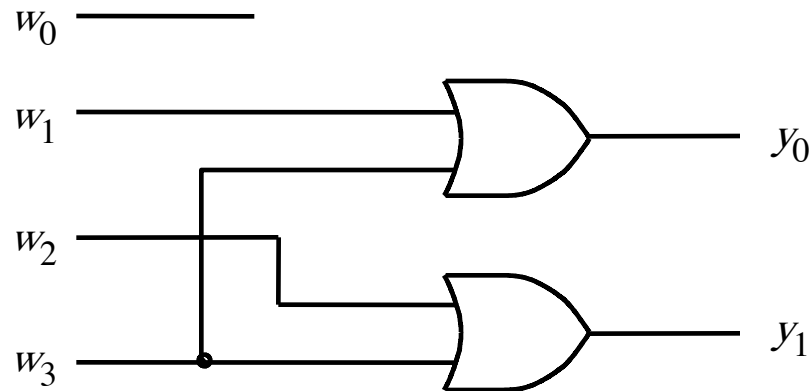

(b) Circuit

# Priority encoders

- In a priority encoder each input has a priority level associated with it
- The encoder outputs indicate the active input that has the highest priority
- Truth table for a 4-to-2 priority encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

- The previous techniques can be used to synthesize the output functions
- However, a more convenient approach is to define intermediate signals

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$

$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

- The outputs can then be written as:

$$y_0 = i_1 + i_3$$


$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$



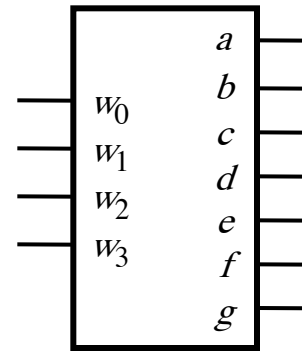
# A BCD-to-7-segment display code converter

- The purpose of decoders and encoders is to convert from one type of input encoding to a different output encoding
- A typical example of a **code converter** is a BCD-to-7-segment decoder, which converts a binary-coded decimal digit into information suitable for driving a digit-oriented display
- A circuit that implements the truth table can be derived using the synthesis techniques previously discussed



(a) Code converter

 

(b) 7-segment display

$w_3$	$w_2$	$w_1$	$w_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

(c) Truth table

# Combinational VHDL

- Non-simple assignment statements
  - Selected assignment
  - Conditional assignment
- Sequential statements
  - If-then-else
  - Case
- Concurrent statements
  - Process vs assignment statements

# VHDL code for a 2-to-1 multiplexer using a selected signal assignment

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;


ENTITY mux2to1 IS
    PORT ( w0, w1, s : IN STD_LOGIC ;
          f : OUT STD_LOGIC ) ;
END mux2to1 ;
```

```
ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
```

```
    WITH s SELECT
        f <= w0 WHEN '0',
          w1 WHEN OTHERS ;
```

```
END Behavior ;
```

 
The “WITH x SELECT” idiom ALWAYS infers a multiplexer. So when your design calls for one, use it!



(a) Graphical symbol

<i>s</i>	<i>f</i>
0	<i>w</i> <sub>0</sub>
1	<i>w</i> <sub>1</sub>

(b) Truth table

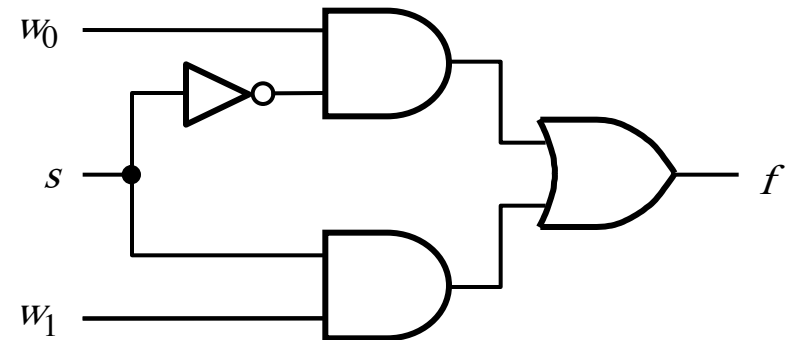

(c) Sum-of-products circuit

All possible valuations of the condition “s” need to be considered

# VHDL code for a 4-to-1 multiplexer

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;


ENTITY mux4to1 IS
    PORT ( w0, w1, w2, w3 : IN      STD_LOGIC ;
           s                : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           f                : OUT     STD_LOGIC ) ;
END mux4to1 ;
```

ARCHITECTURE Behavior OF mux4to1 IS  
BEGIN

WITH s SELECT

f <= w0 WHEN "00",  
w1 WHEN "01",  
w2 WHEN "10",  
w3 WHEN OTHERS ;

END Behavior ;

 

(a) Graphic symbol

s <sub>1</sub>	s <sub>0</sub>	f
0	0	w <sub>0</sub>
0	1	w <sub>1</sub>
1	0	w <sub>2</sub>
1	1	w <sub>3</sub>

(b) Truth table

Note "" used for multi-bit constant;  
" used for single bit constants

# VHDL code for a 4-to-1 multiplexer (cont.)

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
PACKAGE mux4to1_package IS  
    COMPONENT mux4to1  
        PORT ( w0, w1, w2, w3    : IN STD_LOGIC ;  
              s                  : IN STD_LOGIC_VECTOR(1 DOWNTO 0) ;  
              f                  : OUT STD_LOGIC ) ;  
    END COMPONENT ;  
END mux4to1_package ;
```

- Allows us to use the component from the WORK library
- Allows the component to be instantiated within the body of another entity's architecture without a declaration within the header of that architecture

# Hierarchical code for a 16-to-1 MUX


```

1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;
3  LIBRARY work ;      -- this line not really needed for packages
4  USE work.mux4to1_package.all ; -- in the "work"ing directory

5  ENTITY mux16to1 IS
6      PORT (  w : IN STD_LOGIC_VECTOR(0 TO 15) ;
7              s : IN STD_LOGIC_VECTOR(3 DOWNTO 0) ;
8              f : OUT STD_LOGIC ) ;
9  END mux16to1 ;

10 ARCHITECTURE Structure OF mux16to1 IS
11     SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;
12 BEGIN
13     Mux1: mux4to1 PORT MAP ( w(0), w(1), w(2), w(3), s(1 DOWNTO 0), m(0) ) ;
14     Mux2: mux4to1 PORT MAP ( w(4), w(5), w(6), w(7), s(1 DOWNTO 0), m(1) ) ;
15     Mux3: mux4to1 PORT MAP ( w(8), w(9), w(10), w(11), s(1 DOWNTO 0), m(2) ) ;
16     Mux4: mux4to1 PORT MAP ( w(12), w(13), w(14), w(15), s(1 DOWNTO 0), m(3) ) ;
17     Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2), m(3), s(3 DOWNTO 2), f ) ;
18 END Structure ;

```

 

# VHDL code for a 2-to-4 binary decoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY dec2to4 IS
```

```
    PORT ( w   : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
           En  : IN      STD_LOGIC ;
           y   : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
```

```
END dec2to4 ;
```

```
ARCHITECTURE Behavior OF dec2to4 IS
```

```
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
```

```
BEGIN
```

```
    Enw <= En & w ;
```


concatenation

```
    WITH Enw SELECT
```

```
        y <= "1000" WHEN "100",
            "0100" WHEN "101",
            "0010" WHEN "110",
            "0001" WHEN "111",
            "0000" WHEN OTHERS ;
```

<i>En</i>	<i>w</i> <sub>1</sub>	<i>w</i> <sub>0</sub>				
			<i>y</i> <sub>0</sub>	<i>y</i> <sub>1</sub>	<i>y</i> <sub>2</sub>	<i>y</i> <sub>3</sub>
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 

(b) Graphical symbol

```
END Behavior ;
```

# Specification of a 2-to-1 multiplexer using a conditional signal assignment

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT (w0, w1, s      : IN      STD_LOGIC ;
          f              : OUT     STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    f <= w0 WHEN s = '0' ELSE w1 ;
END Behavior ;
```



# VHDL code for a priority encoder

```
LIBRARY ieee ;
```

```
USE ieee.std_logic_1164.all ;
```

```
ENTITY priority IS
```

```
    PORT ( w  : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
```

```
          y  : OUT     STD_LOGIC_VECTOR(1 DOWNT0 0) ;
```

```
          z  : OUT     STD_LOGIC ) ;
```

```
END priority ;
```

```
ARCHITECTURE Behavior OF priority IS
```

```
BEGIN
```

```
    y <= "11" WHEN w(3) = '1' ELSE
```


```
        "10" WHEN w(2) = '1' ELSE
```

```
        "01" WHEN w(1) = '1' ELSE
```

```
        "00" ;
```

```
    z <= '0' WHEN w = "0000" ELSE '1' ;
```

```
END Behavior ;
```

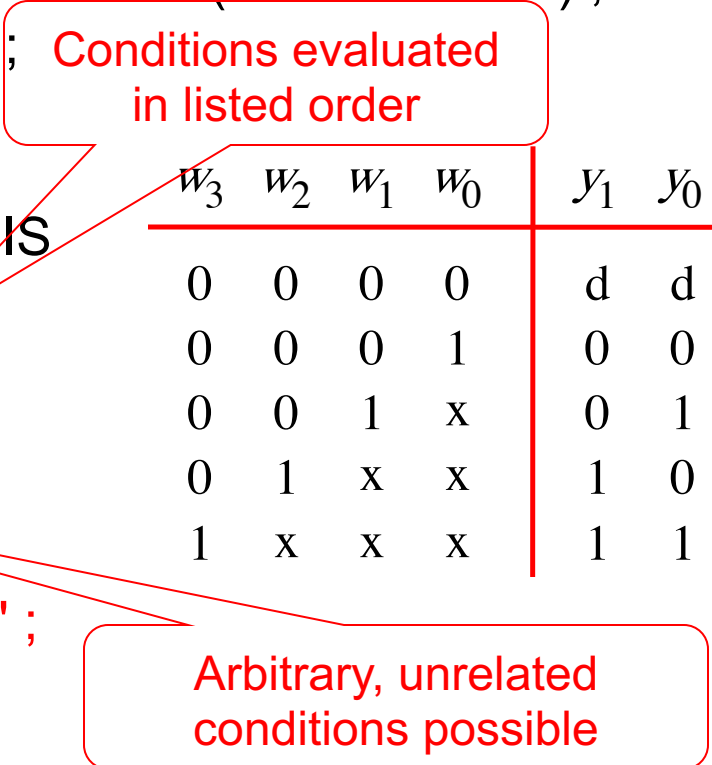

w <sub>3</sub>	w <sub>2</sub>	w <sub>1</sub>	w <sub>0</sub>	y <sub>1</sub>	y <sub>0</sub>	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

# Less efficient code for a priority encoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority IS
    PORT ( w : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          y : OUT      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          z : OUT      STD_LOGIC ) ;
END priority ;

ARCHITECTURE Behavior OF priority IS
BEGIN
    WITH w SELECT
        y <= "00" WHEN "0001",
              "01" WHEN "0010",
              "01" WHEN "0011",
              "10" WHEN "0100",
              "10" WHEN "0101",
              "10" WHEN "0110",
              "10" WHEN "0111",
              "11" WHEN OTHERS ;

    WITH w SELECT
        z <= '0' WHEN "0000",
              '1' WHEN OTHERS ;
END Behavior ;
```

Conditions must be mutually exclusive and are evaluated in parallel

# Code for a 16-to-1 MUX using a generate statement

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE work.mux4to1_package.all ;
```

```
ENTITY mux16to1 IS
```

```
    PORT ( w : IN STD_LOGIC_VECTOR(0 TO 15);  
          s : IN STD_LOGIC_VECTOR(3 DOWNTO 0);  
          f : OUT STD_LOGIC );
```

```
END mux16to1 ;
```

```
ARCHITECTURE Structure OF mux16to1 IS
```

```
    SIGNAL m : STD_LOGIC_VECTOR(0 TO 3);
```

```
BEGIN
```

```
    G1: FOR i IN 0 TO 3 GENERATE
```


```
        Muxes: mux4to1 PORT MAP (
```

```
            w(4*i), w(4*i+1), w(4*i+2), w(4*i+3), s(1 DOWNTO 0), m(i) );
```

```
    END GENERATE ;
```

```
    Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2), m(3), s(3 DOWNTO 2), f );
```

```
END Structure ;
```

 

**FOR...GENERATE statement is used like a macro  
as shorthand to list repeated concurrent statements**

# Hierarchical code for a 4-to-16 binary decoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY dec4to16 IS
```

```
    PORT (    w : IN STD_LOGIC_VECTOR(3 DOWNT0 0) ;
              En : IN STD_LOGIC ;
              y : OUT STD_LOGIC_VECTOR(0 TO 15) ) ;
```

```
END dec4to16 ;
```

```
ARCHITECTURE Structure OF dec4to16 IS
```

```
    COMPONENT dec2to4
```

```
        PORT (    w : IN STD_LOGIC_VECTOR(1 DOWNT0 0) ;
                  En : IN STD_LOGIC ;
                  y : OUT STD_LOGIC_VECTOR(0 TO 3) ) ;
```

```
    END COMPONENT ;
```

```
    SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;
```

```
BEGIN
```

```
    G1: FOR i IN 0 TO 3 GENERATE
```

```
        Dec_right: dec2to4 PORT MAP ( w(1 DOWNT0 0), m(i), y(4*i TO 4*i+3) );
```


```
    G2: IF i=3 GENERATE
```

```
        Dec_left: dec2to4 PORT MAP ( w(3 DOWNT0 2), En, m ) ;
```

```
    END GENERATE ;
```

```
END GENERATE ;
```

```
END Structure ;
```

 

IF...GENERATE statement conditionally instantiates a concurrent statement

# A 2-to-1 MUX specified using an if-then-else statement

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT (w0, w1, s: IN STD_LOGIC ;
          f: OUT STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        IF s = '0' THEN
            f <= w0 ;
        ELSE
            f <= w1 ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Sensitivity  
list

**IMPORTANT!** The assignment to *f* is not committed until the current invocation of the process ends!

- **Processes are typically used to express complex behaviours**
- Processes contain sequential statements i.e statements are evaluated sequentially as opposed to being evaluated concurrently like the previously seen signal assignments
  - *When there are consecutive assignments to the one signal, the last assignment made is the only one that is committed when the process exits*
- A process is triggered when a signal in its sensitivity list has a change in value
  - For combinational processes, the sensitivity list **must include** any signals that appear on the RHS of any assignment statements or that are involved in conditional expressions

# Alternative code for a 2-to-1 multiplexer

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY mux2to1 IS  
    PORT ( w0, w1, s    : IN    STD_LOGIC ;  
          f            : OUT    STD_LOGIC ) ;  
END mux2to1 ;
```

```
ARCHITECTURE Behavior OF mux2to1 IS  
BEGIN
```

```
    PROCESS ( w0, w1, s )  
    BEGIN
```

```
        f <= w0 ;  
        IF s = '1' THEN
```

```
            f <= w1 ;  
        END IF ;
```

```
    END PROCESS ;
```

```
END Behavior ;
```

Works because of  
sequential evaluation

Q1: What is the behaviour of the process if the first assignment statement were moved below the IF statement?

Q2: What is the behaviour if the first assignment statement were removed entirely?

# A priority encoder specified using if-then-else

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY priority IS
  PORT (
    w : IN STD_LOGIC_VECTOR(3 DOWNT0 0) ;
    y : OUT STD_LOGIC_VECTOR(1 DOWNT0 0) ;
    z : OUT STD_LOGIC ) ;
END priority ;
ARCHITECTURE Behavior OF priority IS
BEGIN
  PROCESS ( w )
  BEGIN
    IF w(3) = '1' THEN
      y <= "11" ;
    ELSIF w(2) = '1' THEN
      y <= "10" ;
    ELSIF w(1) = '1' THEN
      y <= "01" ;
    ELSE
      y <= "00" ;
    END IF ;
  END PROCESS ;
  z <= '0' WHEN w = "0000" ELSE '1' ;
END Behavior ;
  
```

w <sub>3</sub>	w <sub>2</sub>	w <sub>1</sub>	w <sub>0</sub>	y <sub>1</sub>	y <sub>0</sub>	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

Note that process statements are concurrently evaluated with all other concurrent statements – ***they are, in effect, a compound form of concurrent statement used to express non-trivial behaviour***

# Alternative code for the priority encoder

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY priority IS  
    PORT ( w : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;  
          y : OUT    STD_LOGIC_VECTOR(1 DOWNTO 0) ;  
          z : OUT    STD_LOGIC ) ;  
END priority ;
```

```
ARCHITECTURE Behavior OF priority IS  
BEGIN
```

```
    PROCESS ( w )  
    BEGIN  
        y <= "00" ;  
        IF w(1) = '1' THEN y <= "01" ; END IF ;  
        IF w(2) = '1' THEN y <= "10" ; END IF ;  
        IF w(3) = '1' THEN y <= "11" ; END IF ;  
  
        z <= '1' ;  
        IF w = "0000" THEN z <= '0' ; END IF ;  
    END PROCESS ;
```

```
END Behavior ;
```

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1



# Code for a one-bit equality comparator

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY compare1 IS
    PORT ( A, B : IN    STD_LOGIC ;
          AeqB : OUT  STD_LOGIC ) ;
END compare1 ;

ARCHITECTURE Behavior OF compare1 IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        AeqB <= '0' ;
        IF A = B THEN
            AeqB <= '1' ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

*Can you visualize  
the resulting  
circuit?*

*Is there a better  
way of specifying  
its behaviour?*


# An example of *incorrect code* that results in implied memory

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY implied IS
    PORT ( A, B : IN    STD_LOGIC ;
          AeqB : OUT   STD_LOGIC ) ;
END implied ;

ARCHITECTURE Behavior OF implied IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        IF A = B THEN
            AeqB <= '1' ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

 The problem arises because we haven't specified a default signal assignment to AeqB i.e. we haven't specified a value for AeqB when  $A \neq B$ .



Resulting circuit has to remember the value of AeqB when either A or B change and  $A \neq B$

# A case statement that represents a 2-to-1 MUX

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux2to1 IS
    PORT ( w0, w1, s : IN    STD_LOGIC ;
           f          : OUT  STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE Behavior OF mux2to1 IS
BEGIN
    PROCESS ( w0, w1, s )
    BEGIN
        CASE s IS
            WHEN '0' =>
                f <= w0 ;
            WHEN OTHERS =>
                f <= w1 ;
        END CASE ;
    END PROCESS ;
END Behavior ;
```

Again, all possible valuations  
of the conditional expression  
need to be catered for

# A 2-to-4 binary decoder

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNT0 0) ;
           En      : IN      STD_LOGIC ;
           y       : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
END dec2to4 ;
```

ARCHITECTURE Behavior OF dec2to4 IS

BEGIN

PROCESS ( w, En )

BEGIN

IF En = '1' THEN

CASE w IS

WHEN "00" => y <= "1000" ;

WHEN "01" => y <= "0100" ;

WHEN "10" => y <= "0010" ;

WHEN OTHERS => y <= "0001" ;

END CASE ;

ELSE

y <= "0000" ;

END IF ;

END PROCESS ;

END Behavior ;

<i>En</i>	<i>w</i> <sub>1</sub>	<i>w</i> <sub>0</sub>	<i>y</i> <sub>0</sub>	<i>y</i> <sub>1</sub>	<i>y</i> <sub>2</sub>	<i>y</i> <sub>3</sub>
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

# Code for a BCD-to-7-segment decoder

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY seg7 IS
    PORT (bcd : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
          leds : OUT    STD_LOGIC_VECTOR(1 TO 7) ) ;
END seg7 ;
ARCHITECTURE Behavior OF seg7 IS
BEGIN

```

```

    PROCESS ( bcd )
    BEGIN

```

```

        CASE bcd IS

```

WHEN "0000"	=> leds	<= "0000001" ;
WHEN "0001"	=> leds	<= "1001111" ;
WHEN "0010"	=> leds	<= "0010010" ;
WHEN "0011"	=> leds	<= "0000110" ;
WHEN "0100"	=> leds	<= "1001100" ;
WHEN "0101"	=> leds	<= "0100100" ;
WHEN "0110"	=> leds	<= "0100000" ;
WHEN "0111"	=> leds	<= "0001111" ;
WHEN "1000"	=> leds	<= "0000000" ;
WHEN "1001"	=> leds	<= "0001100" ;
WHEN OTHERS	=> leds	<= "-----" ;

```

        END CASE ;

```

```


    END PROCESS ;

```


```

END Behavior ;

```

 

-- abcdefg - common anode

 

7-segment display

# Specifying the functionality of a 74381 ALU chip

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
ENTITY alu IS
    PORT ( s : IN STD_LOGIC_VECTOR(2 DOWNT0 0) ;
          A, B : IN STD_LOGIC_VECTOR(3 DOWNT0 0) ;
          F : OUT STD_LOGIC_VECTOR(3 DOWNT0 0) ) ;
END alu ;

```

```

ARCHITECTURE Behavior OF alu IS
BEGIN

```

```

    PROCESS ( s, A, B )
    BEGIN
        CASE s IS
            WHEN "000" =>
                F <= "0000" ;
            WHEN "001" =>
                F <= B - A ;
            WHEN "010" =>
                F <= A - B ;
            WHEN "011" =>
                F <= A + B ;

```

Operation	Inputs			Outputs F
	$s_2$	$s_1$	$s_0$	
Clear	0	0	0	0 0 0 0
B−A	0	0	1	$B - A$
A−B	0	1	0	$A - B$
ADD	0	1	1	$A + B$
XOR	1	0	0	$A \text{ XOR } B$
OR	1	0	1	$A \text{ OR } B$
AND	1	1	0	$A \text{ AND } B$
Preset	1	1	1	1 1 1 1

```

        WHEN "100" =>
            F <= A XOR B ;
        WHEN "101" =>
            F <= A OR B ;
        WHEN "110" =>
            F <= A AND B ;
        WHEN OTHERS =>
            F <= "1111" ;
    END CASE ;
END PROCESS ;
END Behavior ;

```

# VHDL operators used for synthesis

Table 6.2. VHDL operators (used for synthesis).

Operator category	Operator symbol	Operation performed
Logical	AND OR NAND NOR XOR XNOR NOT	AND OR Not AND Not OR XOR Not XOR NOT
Relational	= /= > < >= <=	Equality Inequality Greater than Less than Greater than or equal to Less than or equal to
Arithmetic	+ - * /	Addition Subtraction Multiplication Division
Concatenation	&	Concatenation
Shift and Rotate	SLL SRL SLA SRA ROL ROR	Shift left logical Shift right logical Shift left arithmetic Shift right arithmetic Rotate left Rotate right

- Precedence in the table to the left is from top to bottom between categories
- Operators within the same category have the same precedence and are therefore evaluated from left to right
- Often good to parenthesize expressions to explicitly confirm evaluation order
- Note also that  

$$s \leq a + b + c + d;$$
 results in 3 sequential additions, whereas  

$$s \leq (a + b) + (c + d);$$
 performs two sub-additions in parallel and then one final addition for 2/3 the delay

# Examples



# Brown & Vranesic: Example 6.25

## Problem:

Implement the function  $f(w_1, w_2, w_3) = \sum m(0, 1, 3, 4, 6, 7)$  using a 3-to-8 binary decoder and an OR gate

# Example 6.27

## Problem:

Implement the function

$$f = \overline{w_1}\overline{w_2}\overline{w_4}\overline{w_5} + w_1w_2 + w_1w_3 + w_1w_4 + w_3w_4w_5$$


using a 4-to-1 multiplexer and as few gates as possible.

Assume that only the uncomplemented inputs are available as inputs.

# Example 6.27
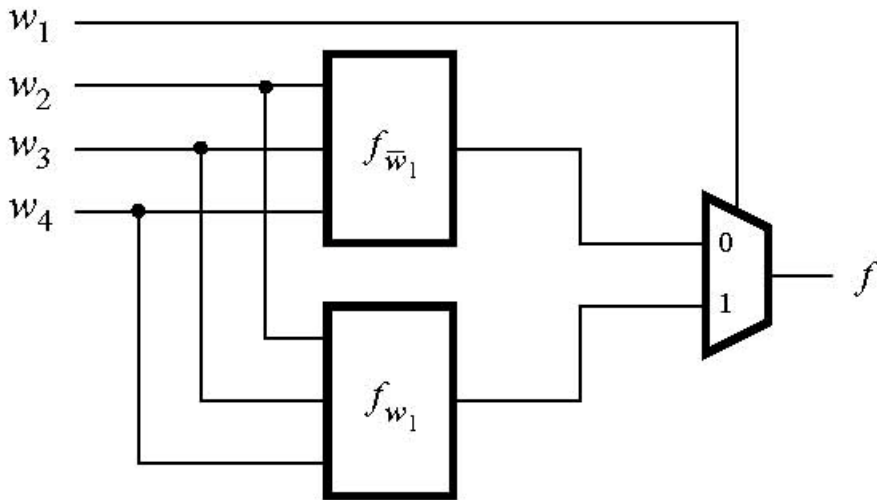
# Example 6.29

- For a four-variable function,  $f(w_1, \dots, w_4)$ , Shannon's expansion with respect to  $w_1$  is  $f = \overline{w_1}f_{\overline{w_1}} + w_1f_{w_1}$ , which can be implemented as in circuit (a):




(a) Shannon's expansion of the function  $f$ .

## Problem 1:

If the composition yields  $f_{\overline{w_1}} = 0$  then the multiplexer in figure (a) can be replaced by a single logic gate. Show this circuit.
 
# Example 6.29

- For a four-variable function,  $f(w_1, \dots, w_4)$ , Shannon's expansion with respect to  $w_1$  is  $f = \overline{w_1}f_{\overline{w_1}} + w_1f_{w_1}$ , which can be implemented as in circuit (a):



(a) Shannon's expansion of the function  $f$ .

## Problem 2:


If the composition yields  $f_{w_1} = 1$  then the multiplexer in figure (a) can be replaced by a single logic gate. Show this circuit.

# Example 6.31
 
## Problem:

Design a circuit that can shift a 4-bit vector  $W = w_3w_2w_1w_0$  one bit position to the right when a control signal *Shift* is equal to 1.


Let the outputs of the circuit be  $Y = y_3y_2y_1y_0$  and a signal  $k$ , such that if *Shift* = 1 then  $y_3 = 0$ ,  $y_2 = w_3$ ,  $y_1 = w_2$ ,  $y_0 = w_1$ , and  $k = w_0$ . If *Shift* = 0, then  $Y = W$  and  $k = 0$ .



# 4-bit Barrel Shifter

$s_1$	$s_0$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	$w_3$	$w_2$	$w_1$	$w_0$
0	1	$w_0$	$w_3$	$w_2$	$w_1$
1	0	$w_1$	$w_0$	$w_3$	$w_2$
1	1	$w_2$	$w_1$	$w_0$	$w_3$

(a) Truth table

 

(b) Circuit

# VHDL code for the shifter of Example 6.31

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY shifter IS
```

```
    PORT ( w      : IN    STD_LOGIC_VECTOR(3 DOWNT0 0) ;  
          Shift   : IN    STD_LOGIC ;  
          y      : OUT   STD_LOGIC_VECTOR(3 DOWNT0 0) ;  
          k      : OUT   STD_LOGIC ) ;
```

```
END shifter ;
```

```
ARCHITECTURE Behavior OF shifter IS
```

```
BEGIN
```

```
    PROCESS (Shift, w)
```

```
    BEGIN
```

```
        IF Shift = '1' THEN
```

```
            y(3) <= '0' ;
```

```
            y(2 DOWNT0 0) <= w(3 DOWNT0 1) ;
```

```
            k <= w(0) ;
```

```
        ELSE
```


```
            y <= w ;
```

```
            k <= '0' ;
```

```
        END IF ;
```

```
    END PROCESS ;
```

```
END Behavior ;
```

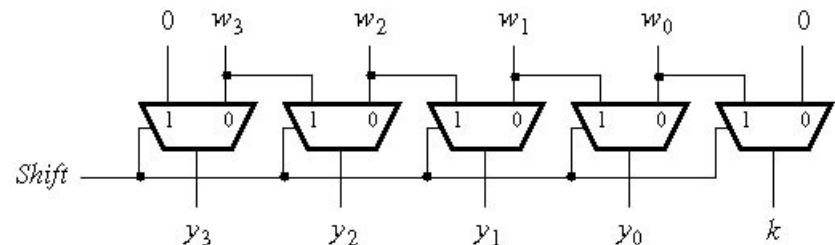



# Alternative code using SRL op

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.numeric_std.all ;

ENTITY shifter IS
    PORT ( w      : IN    UNSIGNED(3 DOWNTO 0) ;
          Shift   : IN    STD_LOGIC ;
          y       : OUT   UNSIGNED(3 DOWNTO 0) ;
          k       : OUT   STD_LOGIC ) ;
END shifter ;
```

ARCHITECTURE Behavior OF shifter IS

```
BEGIN
    PROCESS (Shift, w)
    BEGIN
        IF Shift = '1' THEN
            y <= w SRL 1 ;
            k <= w(0) ;
        ELSE
            y <= w ;
            k <= '0' ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

